

Study Material

Text Book

Elements of Electromagnetics, 6th Ed.
Matthew N. O. Sadiku
Oxford University Press

Study Smith Charts

Read Chapter 11, pp. 554–574.
Read “Smith Charts” notes from course website.

Problems

Problem #1

At some distance away from the load along a 50Ω transmission line, the input impedance is measured to be $50 + j50 \Omega$. What is the input admittance at this point? Perform the calculation by hand and by using a Smith chart.

Problem #2

A length of 50Ω transmission line is connected to a load and the input impedance is measured to be $100 + j50 \Omega$. Determine the input impedance at a distance 0.2λ toward the source from this point using a Smith chart.

Problem #3

A 75Ω transmission line is connected to a load with complex impedance of $Z_L = 22.5 + j30 \Omega$. Use a Smith Chart to determine the corresponding load admittance as well as the VSWR on the transmission line. Verify your results by hand.

Problem #4

A lossless transmission line has distributed parameters $C = 120 \text{ pF/m}$ and $L = 300 \text{ nH/m}$. It operates at 10 GHz and is connected to a 6.97 pF capacitor as the load. Use a Smith chart to calculate the input impedance 5.6 mm from the load. Also determine the VSWR of the circuit. Compare your answers to results calculated by hand.