

### Problem #1: Complex Propagation Constant

The complex propagation constant  $\gamma$  is related to the lumped element transmission line parameters  $R$ ,  $L$ ,  $G$ , and  $C$  through the following equation.

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

From this equation, derive the following expressions for the attenuation coefficient  $\alpha$  and the propagation constant  $\beta$  in terms of just  $R$ ,  $L$ ,  $G$ , and  $C$ .

$$\alpha = \sqrt{\frac{1}{2} \left[ RG - \omega^2 LC + \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)} \right]}$$
$$\beta = \sqrt{\frac{1}{2} \left[ -RG + \omega^2 LC + \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)} \right]}$$

### Problem #2: Complex Impedance

The transmission line equations can be written as

$$-\frac{dV(z)}{dz} = (R + j\omega L)I(z) \quad -\frac{dI(z)}{dz} = (G + j\omega C)V(z)$$

Given that the definition of the characteristic impedance of a transmission line is  $Z_0 = V_0^+ / I_0^+$ , derive the following expression for  $Z_0$  in terms of just  $R$ ,  $L$ ,  $G$ , and  $C$ .

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

### Problem #3: Impedance Transformation

A lossless transmission line with  $C = 24$  pF/m and  $L = 60$  nH/m operates at 5.0 GHz and is connected to a 100 nF capacitor as the load.

- What is the input impedance of the transmission line if its length is 4.0 cm?
- Is the input impedance inductive, capacitive, or resistive?
- What value inductor, capacitor, or resistor does the input impedance act like?

### Problem #4: Reflections

A 50  $\Omega$  transmission line is connected to an antenna with a 72  $\Omega$  input impedance.

- What is the reflection coefficient from the antenna?
- What fraction of power is fed into the antenna?
- What is the voltage standing wave ratio (VSWR) in the transmission line feeding the antenna?
- What can be done to deliver power to the antenna more efficiently? List as many solutions as possible and be specific.