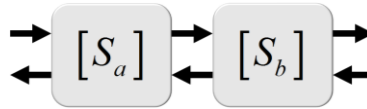


Problem #1: Cascading Two [S] Matrices

Two two-port networks (A and B) are to be connected in series as illustrated below.



Each network is described by its own set of four scattering parameters as expressed in Eq. (1).

$$[S_a] = \begin{bmatrix} S_{11}^a & S_{12}^a \\ S_{21}^a & S_{22}^a \end{bmatrix} \quad [S_b] = \begin{bmatrix} S_{11}^b & S_{12}^b \\ S_{21}^b & S_{22}^b \end{bmatrix} \quad (1)$$


Derive expressions to calculate the four scattering parameters S_{11} , S_{12} , S_{21} , and S_{22} of the combined network. This is NOT simple matrix multiplication.

$$[S] = [S_a] \otimes [S_b] = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \quad (2)$$

Show all of your steps in detail and simplify your final expressions as much as possible.

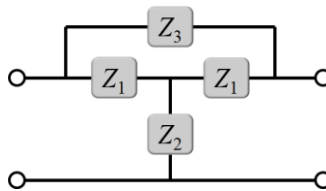Problem #2: Impedance and Admittance Matrices

A two-port network is composed of four impedance elements as shown in the circuit below.



Part (a)

Derive the admittance matrix $[Y]$ for this network as a function of the impedance elements in this circuit Z_1 , Z_2 , and Z_3 . Show all your work. You may use computer software to derive symbolic solutions to the matrix inverses if you wish.

Part (b)

Similarly, derive the corresponding impedance matrix $[Z]$ for this network as a function of the impedance elements in this circuit Z_1 , Z_2 , and Z_3 . Show all your work.

Problem #3: Power

A two-port network is formed from two shunt 5Ω resistors separated by a quarter-wavelength length of lossless 100Ω transmission line. This network is inserted between a source and load which both have an impedance of 50Ω . Draw the circuit and calculate the transducer and dissipative losses of the network in decibels.