




# NETWORK MATRICES

## EE 4380/5390 Microwave Engineering

Pioneering 21<sup>st</sup> Century  
Electromagnetics and Photonics

<http://emlab.utep.edu/>

### N-Port Networks

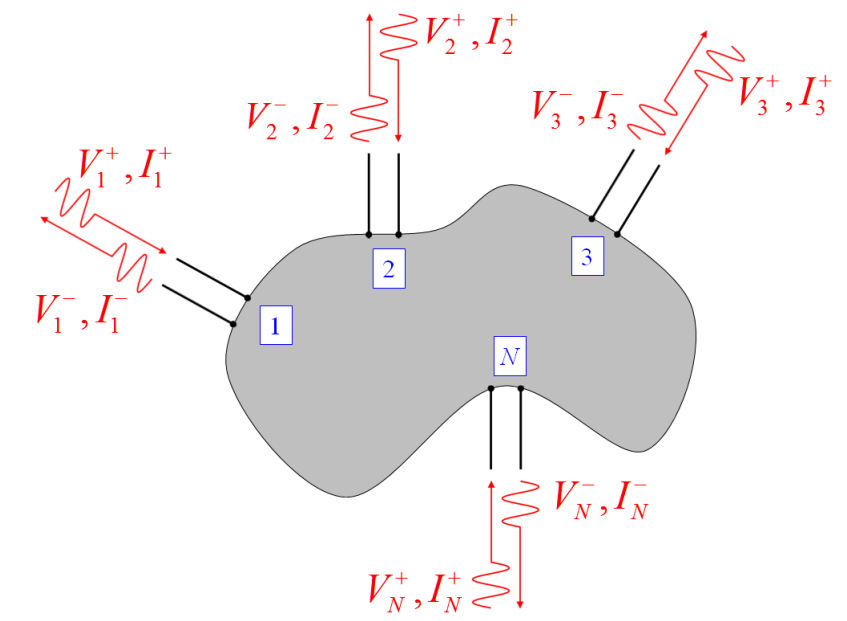

#### Total Voltage and Current

$$V_n = V_n^+ + V_n^- \quad I_n = I_n^+ - I_n^-$$

$V_n^+$  &  $I_n^+$   $\equiv$  forward waves  
 $V_n^-$  &  $I_n^-$   $\equiv$  backward waves

### Terms

**Impedance**  
 $Z = R + jX$       $R \equiv$  resistance  
                                $X \equiv$  reactance

$Z(-\omega) = Z^*(\omega)$      Hermitian  
 $R(-\omega) = R(-\omega)$      even  
 $X(-\omega) = -X(\omega)$      odd  
 $|\Gamma(-\omega)| = |\Gamma(\omega)|$      even

**Admittance**  
 $Y = G + jB$       $G \equiv$  conductance  
                                $B \equiv$  susceptance  
 $Y = Z^{-1}$

**Foster's Reactance Thm.**

$$\frac{\partial X}{\partial \omega} > 0 \quad \text{and} \quad \frac{\partial B}{\partial \omega} > 0$$

### ABCD Matrix [T]

**Definition**


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$      open circuit voltage ratio  
 $B = \left. \frac{V_1}{I_2} \right|_{V_2=0}$      short circuit transfer impedance  
 $C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$      open circuit transfer impedance  
 $D = \left. \frac{I_1}{I_2} \right|_{V_2=0}$      short circuit current ratio

**Reciprocal**  
 $\det[T] = 0$

**Lossless**  
 $\text{Im}(A) = \text{Re}(B) = \text{Re}(C) = \text{Im}(D) = 0$

**Cascading**

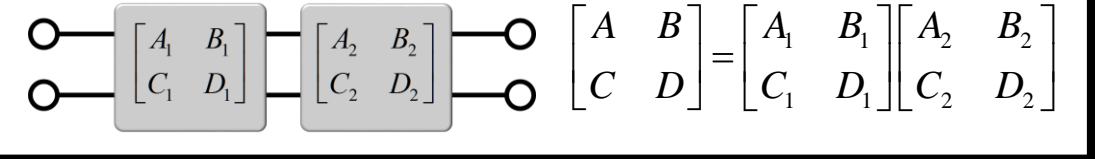

### Scattering Matrix [S]

**Definition**

$$\begin{bmatrix} V_1^- \\ V_2^- \\ \vdots \\ V_N^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \dots & S_{1N} \\ S_{21} & S_{22} & \dots & S_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ S_{N1} & S_{N2} & \dots & S_{NN} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \\ \vdots \\ V_N^+ \end{bmatrix}$$

$S_{ij} = \left. \frac{V_i^-}{V_j^+} \right|_{\text{no other applied voltages}}$

**Reciprocal**     **Lossless**  
 $[S] = [S]^T$       $[S]$  is unitary

**Cascading**

$$[S_{AB}] = [S_A] \otimes [S_B]$$

$$[S_{AB}] = \frac{1}{1 - S_{22}^A S_{11}^B} \begin{bmatrix} S_{11}^A - S_{11}^B \det[S_A] & S_{12}^A S_{12}^B \\ S_{21}^A S_{21}^B & S_{22}^B - S_{22}^A \det[S_B] \end{bmatrix}$$



### Impedance Matrix [Z]

**Definition**

$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & \dots & Z_{1N} \\ Z_{21} & Z_{22} & \dots & Z_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ Z_{N1} & Z_{N2} & \dots & Z_{NN} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix}$$

$Z_{ij} = \left. \frac{V_i}{I_j} \right|_{\text{all other currents zero}}$

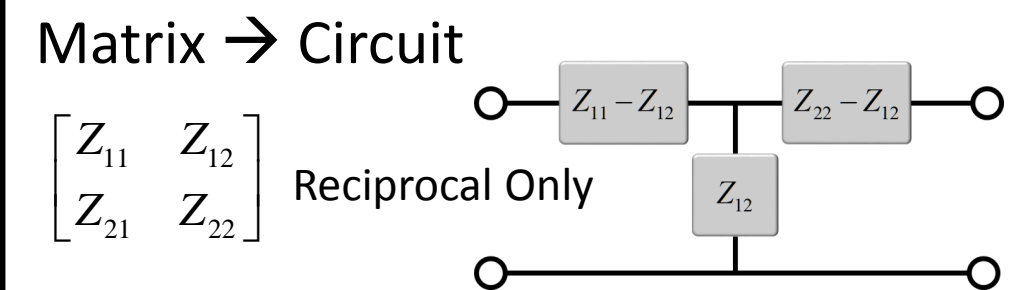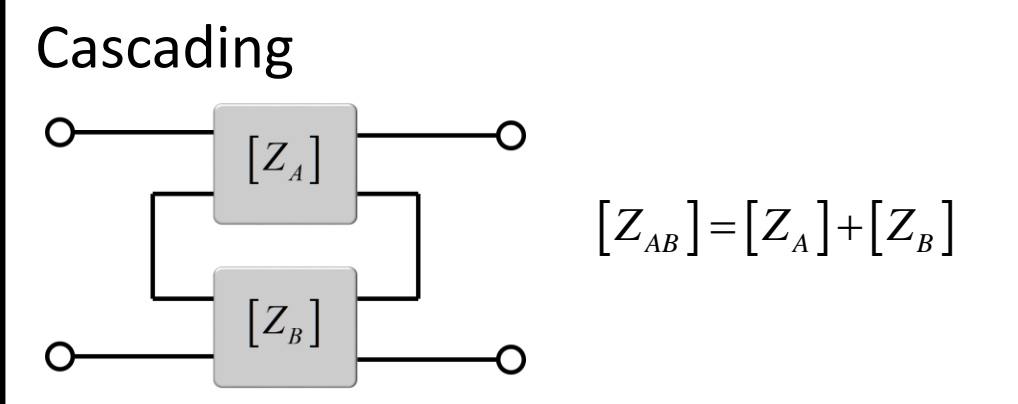**Reciprocal**     **Lossless**  
 $[Z] = [Z]^T$       $\text{Re}\{Z_{ij}\} = 0$





### Admittance Matrix [Y]

**Definition**

$$\begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & \dots & Y_{1N} \\ Y_{21} & Y_{22} & \dots & Y_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ Y_{N1} & Y_{N2} & \dots & Y_{NN} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix}$$

$Y_{ij} = \left. \frac{I_i}{V_j} \right|_{\text{all other voltages zero}}$

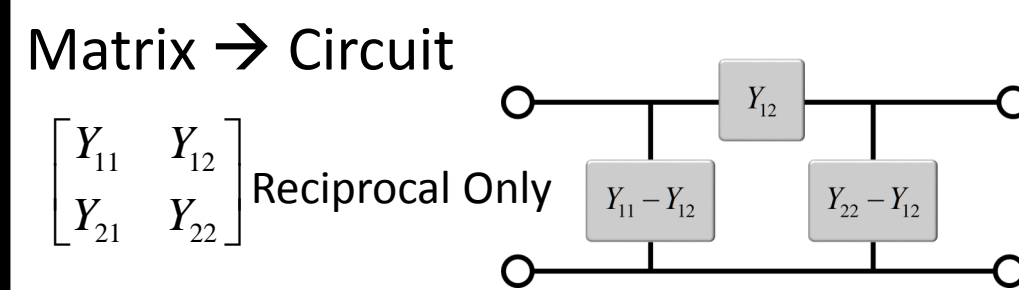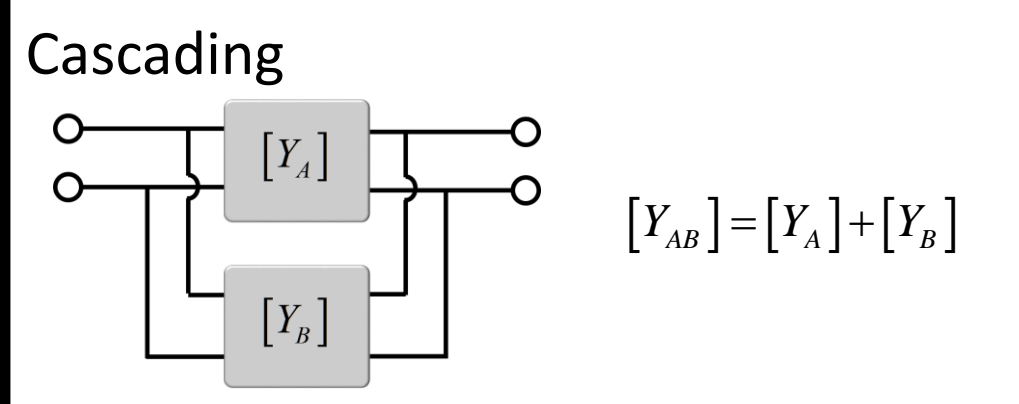**Reciprocal**     **Lossless**  
 $[Y] = [Y]^T$       $\text{Re}\{Y_{ij}\} = 0$



### Performance Metrics Through Network

**Input Impedance**     **Conjugate Matching**     **Max Available Power**

$$Z_{in} = \frac{AZ_L + B}{CZ_L + D}$$

$Z_L = Z_s^*$       $P_A = \frac{|V_s|^2}{8R_s}$  when  $Z_L = Z_s^*$

$R_L = R_s$       $X_L = -X_s$

**Input Reflection**

$$\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$$

**Average Power to Load**

$$P_L = \frac{|V_s|^2}{8Z_0} \frac{|S_{21}|^2 (1 - |\Gamma_L|^2) |1 - \Gamma_s|^2}{|1 - S_{22}\Gamma_L|^2 |1 - \Gamma_s\Gamma_{in}|^2}$$

**Insertion Loss**

$$L_I = 10 \log_{10} \left| \frac{AZ_L + B + CZ_s Z_L + DZ_s}{Z_s + Z_L} \right|^2$$

**Insertion Phase**

$$\phi_I = \tan^{-1} \left( \frac{\text{Im}[AZ_L + B + CZ_s Z_L + DZ_s]}{\text{Re}[AZ_L + B + CZ_s Z_L + DZ_s]} \right)$$

**Transducer Loss**

$$L_T = 10 \log_{10} \left( \frac{|AZ_L + B + CZ_s Z_L + DZ_s|^2}{4R_s R_L} \right)$$

**Gain through Network**

$$G = \frac{P_L}{P_{in}} = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{|1 - S_{22}\Gamma_L|^2 (1 - |\Gamma_{in}|^2)}$$

**Mismatch Loss**

$$L_M = 10 \log_{10} \left( \frac{1}{1 - |\Gamma_{in}|^2} \right)$$

**Loss Term Relation**

$$L_T = L_M + L_\sigma$$

$L_\sigma \equiv$  dissipative loss