



Electromagnetics:
Electromagnetic Field Theory

Analysis & Design of Multi-Segment Transmission Lines

1

Lecture Outline


- Circuit/Wave Equivalence
- Analysis of Multi Segment Transmission Lines
- Digital Filter Analogy
- Example

2

Circuit Wave Equivalence

3


Circuit/Wave Equivalence (1 of 3)

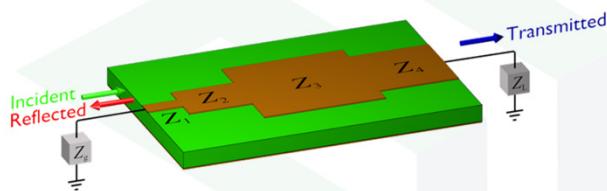

Here we have a “stepped-impedance” microwave circuit.

4


Circuit/Wave Equivalence (2 of 3)

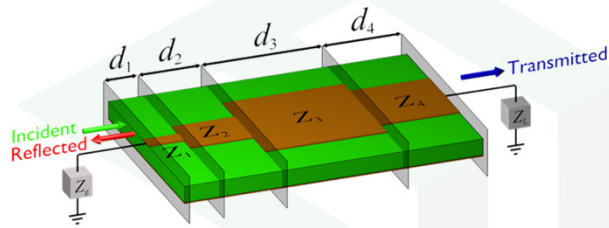

We view the circuit as a series of discrete segments that are uniform within the segment.

5

Circuit/Wave Equivalence (3 of 3)

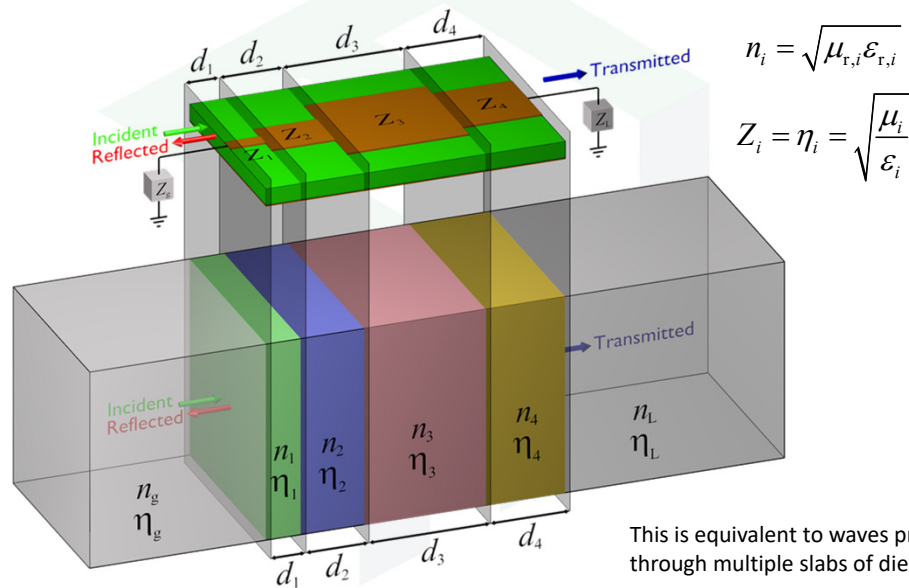


This is equivalent to waves propagating through multiple slabs of dielectric.

6

Analysis of Multi-Segment Transmission Lines

7


Impedance Transformation Method (1 of 6)

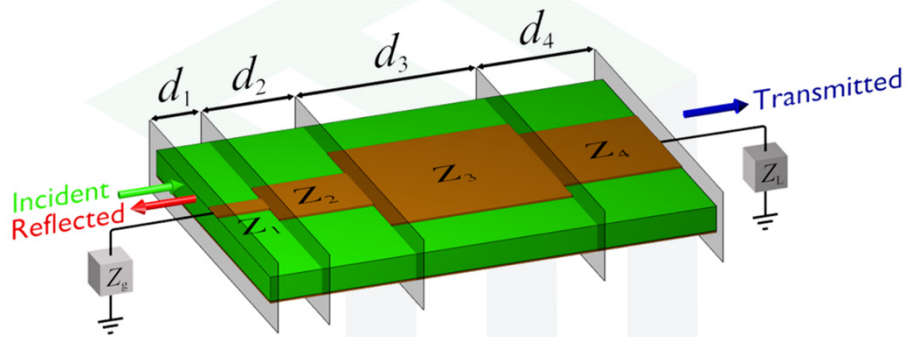

How do we calculate the reflection from this circuit?


8

Impedance Transformation Method (2 of 6)

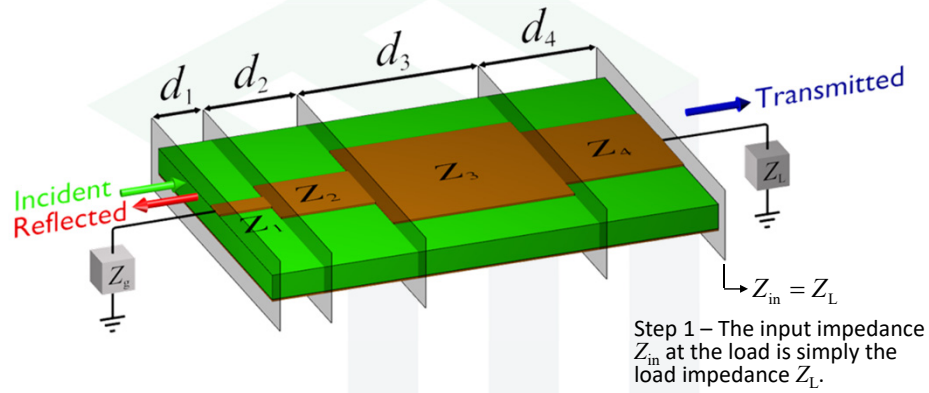


9

Impedance Transformation Method (3 of 6)

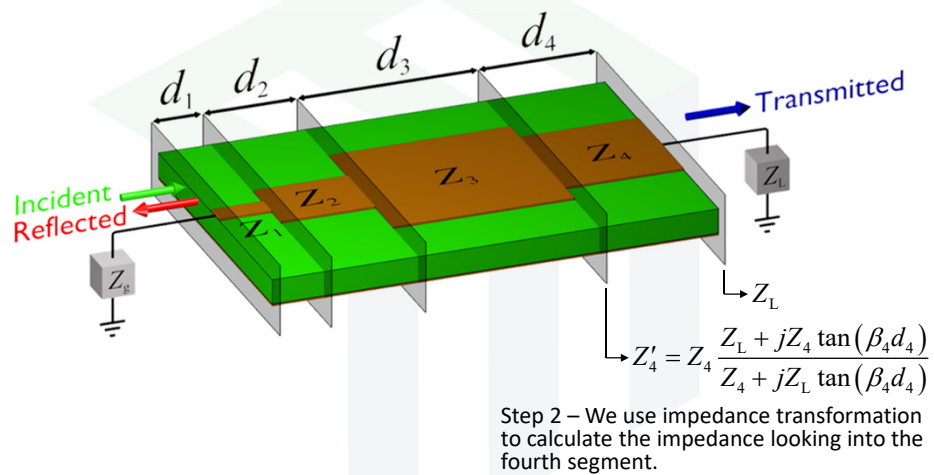

10


Impedance Transformation Method (4 of 6)

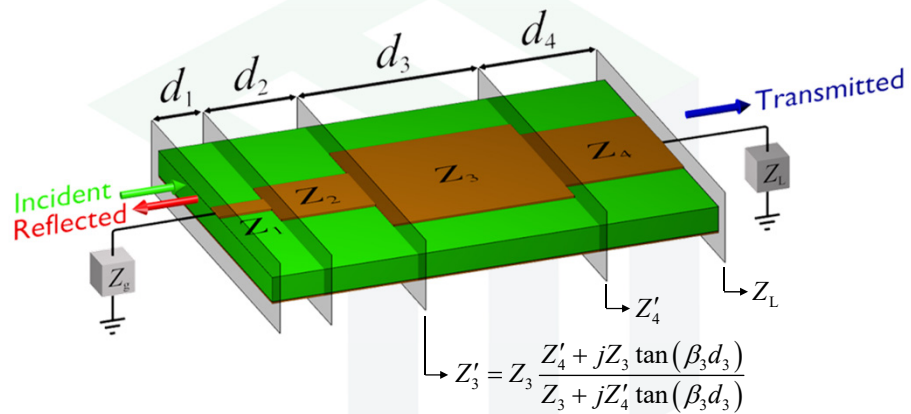

Step 3 – We use impedance transformation to calculate the impedance looking into the third segment.

11


Impedance Transformation Method (5 of 6)

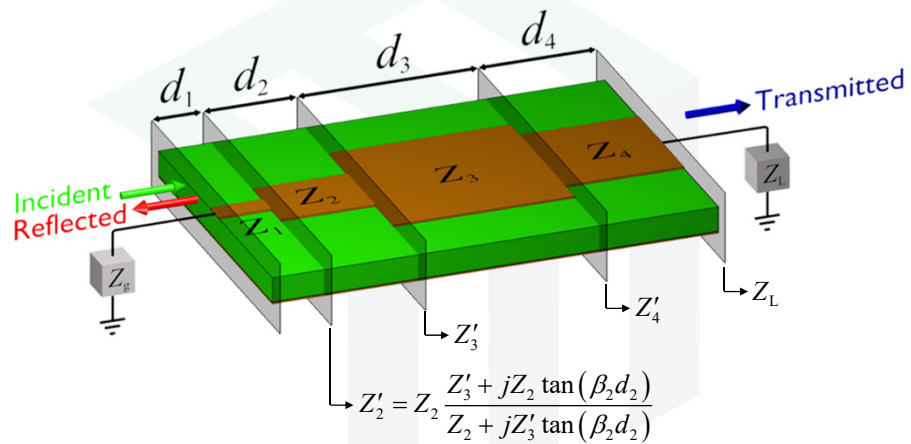

Step 4 – We use impedance transformation to calculate the impedance looking into the second segment.


12

Impedance Transformation Method (6 of 6)

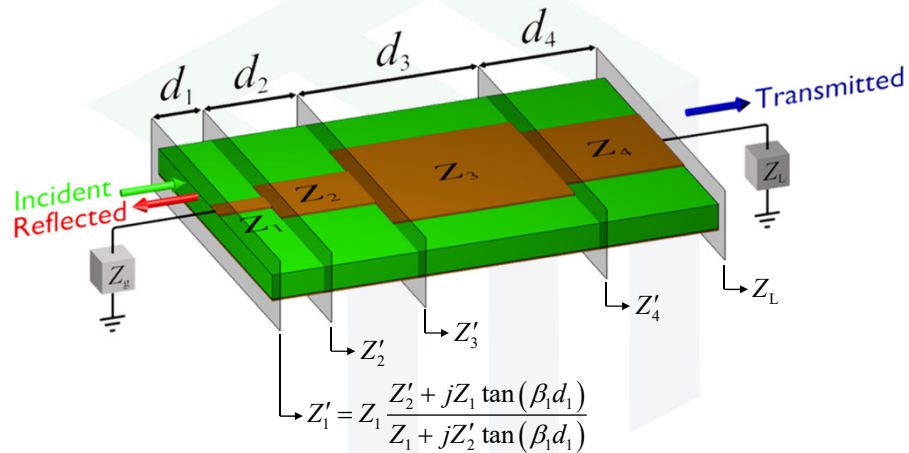

Step 5 – We use impedance transformation to calculate the impedance looking into the first segment.

Impedance Transformation Method (7 of 6)

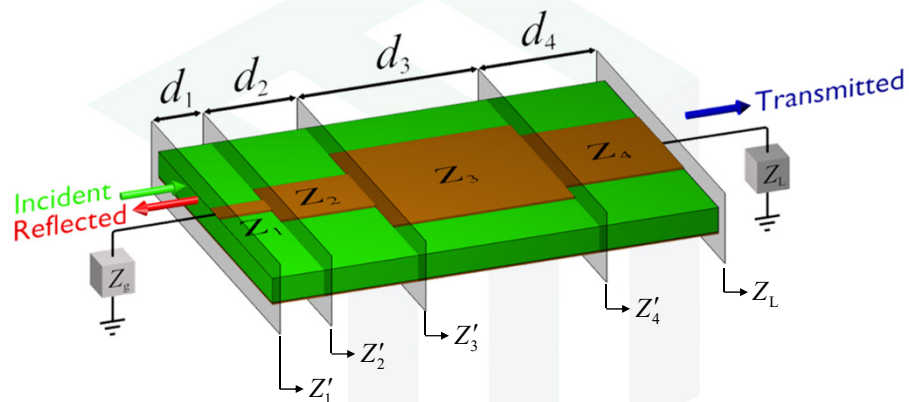


Step 6 – We calculate the overall reflection as seen by the generator.

$$\Gamma = \frac{Z'_1 - Z_g}{Z'_1 + Z_g}$$

It is straightforward to extend this procedure to analyze circuits composed of any number of segments.

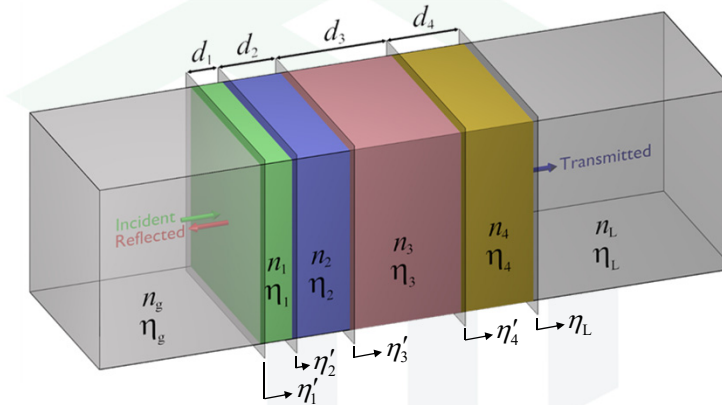Impedance Transformation Method for Waves



Impedance Transformation for Waves

$$\eta'_i = \eta_i \frac{\eta'_{i+1} + j\eta_i \tan(\beta_i d_i)}{\eta_i + j\eta'_{i+1} \tan(\beta_i d_i)}$$

Overall Reflection

$$r = \frac{\eta'_1 - \eta_g}{\eta'_1 + \eta_g}$$

$$R = |r|^2$$

Notes on the Impedance Transformation Method

- Very fast and simple to implement!
- Difficult to modify the method to calculate transmission when the materials have loss or gain.
- When gain and loss can be ignored, $R + T = 1$.
- Method cannot directly visualize the fields inside of the device.

Digital Filter Analogy

Slide 17

17

Conditions for Analogy

The reflection coefficient Γ_i for a wave in medium i incident on medium $i+1$ is given by

$$\Gamma_i = \frac{Z_{i+1} - Z_i}{Z_{i+1} + Z_i} = \frac{\eta_{i+1} - \eta_i}{\eta_{i+1} + \eta_i}$$

Notice this is written for both transmission lines and dielectric slabs.

The overall reflection coefficient Γ_{in} from a series of M segments is very complicated. However, it can be greatly simplified given two conditions:

1. The electrical length of each segment is the same.

$$\psi \cong \beta_1 d_1 \cong \dots \cong \beta_M d_M$$

2. The reflection coefficients Γ_i at the interfaces are small, allowing us to ignore waves reflected more than once.

$$|\Gamma_i| < \sim 0.1$$

Slide 18

18

Expression for Overall Reflection

Given the two conditions on the previous slide, the overall reflection coefficient Γ_{in} from M layers can be written as

$$\Gamma_{\text{in}} = \Gamma_0 + \Gamma_1 e^{-j2\psi} + \Gamma_2 e^{-j4\psi} + \dots + \Gamma_M e^{-j2M\psi}$$

$$\Gamma_i = \frac{Z_{i+1} - Z_i}{Z_{i+1} + Z_i} = \frac{\eta_{i+1} - \eta_i}{\eta_{i+1} + \eta_i} \quad \psi \cong \beta_1 d_1 \cong \dots \cong \beta_M d_M$$

Digital FIR Filters

The general form of the transfer function for a finite impulse response (FIR) digital filter is

$$H(z) = \sum_{k=0}^M h(k) z^{-k} = h(0) + h(1)z^{-1} + h(2)z^{-2} + \dots + h(M)z^{-M}$$

If we excite the digital filter with an impulse function at $t = 0$, then we observe $h(0)$ at time 0, $h(1)$ at time 1, $h(2)$ at time 2, and so on.

The frequency-domain response of a digital FIR filter is

$$H(\omega) = \sum_{k=0}^M h(k) e^{-j2k\psi} = h(0) + h(1)e^{-j2\psi} + h(2)e^{-j4\psi} + \dots + h(M)e^{-j2M\psi}$$

The Analogy

If we compare the overall reflection coefficient Γ_{in} of our multi-segment/multi-layer device, we see that it has the same form as a digital filter.

$$\Gamma_{\text{in}} = \Gamma_0 + \Gamma_1 e^{-j2\psi} + \Gamma_2 e^{-j4\psi} + \dots + \Gamma_M e^{-j2M\psi}$$

$$H = h(0) + h(1) e^{-j2\psi} + h(2) e^{-j4\psi} + \dots + h(M) e^{-j2M\psi}$$


This means we can design multi-segment/multi-layer filters just like we design a digital filter.

Much is known about designing digital filters and all of this knowledge and all of the tools can be used to design filters for electromagnetic waves!

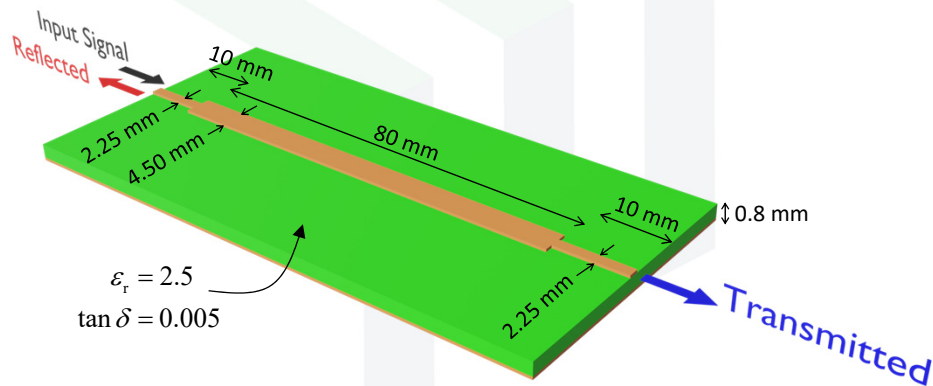Example

Stepped-Impedance Microstrip


A stepped impedance microstrip circuit is designed into an FR4 printed circuit board as illustrated below. Simulate its reflectance and transmittance from 0 GHz up to 10 GHz.



23

Step 1 – Analyze TL Regions

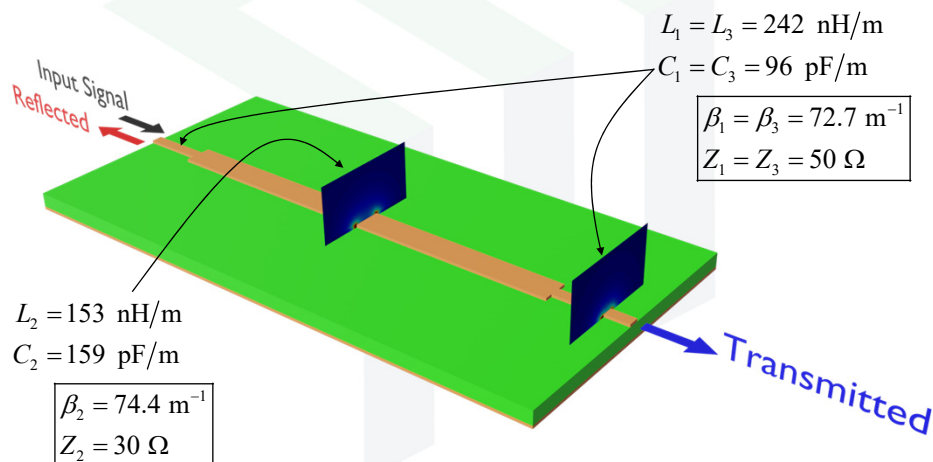An electromagnetic simulation is performed to calculate the parameters characterizing the transmission lines in each segment of the filter.




24

Step 2 – Simulate Multi-Segment Device

Simulation (1D): ~10 sec

Simulation (3D): ~4 min

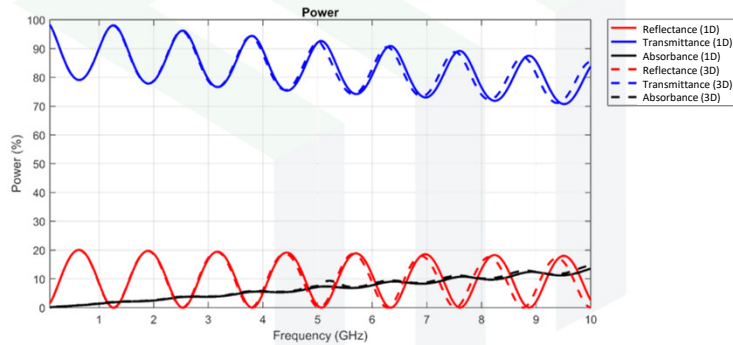

Each frequency ω is an entirely different simulation.
 β must be recalculated at each frequency ω .

$$\beta_i = \omega \sqrt{L_i C_i}$$