


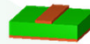
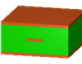
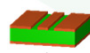
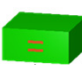





Computational Science:  
Computational Methods in Engineering

## Transmission Lines



### What Are Transmission Lines?


	Homogeneous	Inhomogeneous
Single-Ended	 coaxial	 microstrip
	 stripline	 coplanar
Differential	 buried parallel plate	 coplanar strips
	 shielded pair	 slotline

Transmission lines are essentially high-frequency electrical cables composed of two or more metal wires.


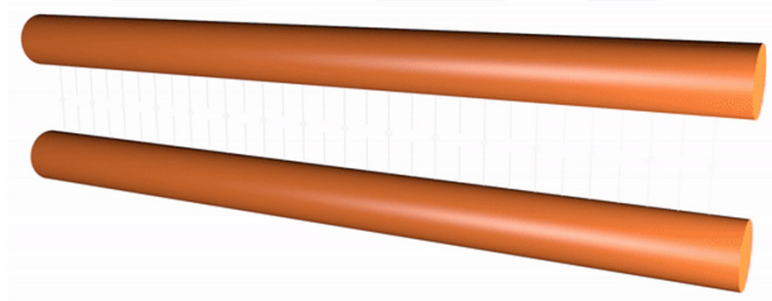
## Transmission Line Parameters RLGC


Think of transmission lines as being composed of millions of tiny little circuit elements that are distributed along the length of the line.



In fact, these circuit elements are not discrete, but continuous along the length of the transmission line.
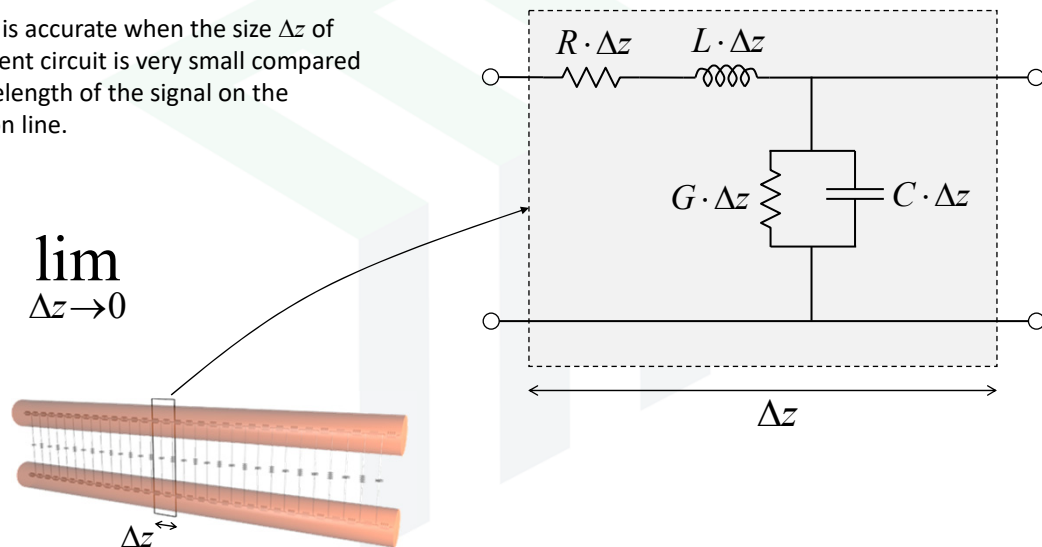
## RLGC Circuit Model

This model is accurate when the size  $\Delta z$  of the equivalent circuit is very small compared to the wavelength of the signal on the transmission line.



## Distributed TL Parameters

### Distributed Circuit Parameters

$R$  ( $\Omega/\text{m}$ )

Resistance per unit length. Arises due to resistivity in the conductors.

$L$  (H/m)

Inductance per unit length. Arises due to stored magnetic energy around the line.

$G$  ( $1/\Omega\cdot\text{m}$ )


Conductance per unit length. Arises due to conductivity in the dielectric separating the conductors.

$$G \neq \frac{1}{R}$$

$C$  (F/m)

Capacitance per unit length. Arises due to stored electric energy between the conductors.

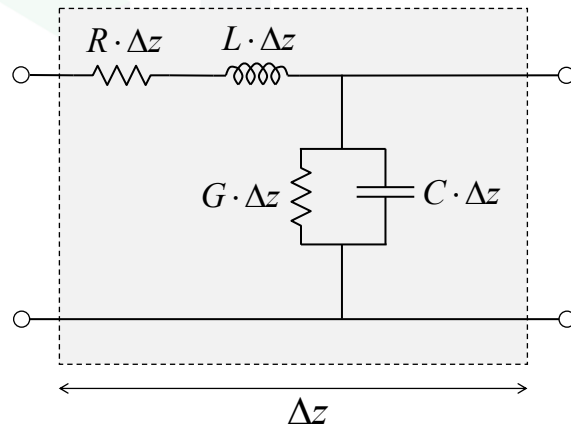There are many possible circuit models for transmission lines, but most produce the same equations after analysis.



## Characteristic Impedance, $Z_0$

The characteristic impedance is the voltage divided the current at any point along the transmission line.

$$Z_0 = \frac{V}{I}$$

After analyzing the equivalent circuit, the characteristic impedance is derived to be


$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

When loss is ignored (usually very accurate to do this), the above equation reduces to

$$Z_0 = \sqrt{\frac{L}{C}}$$

## Example RLGC Parameters

**RG-59 Coax**

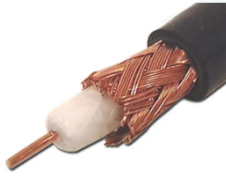


$$\begin{aligned} R &= 36 \text{ m}\Omega/\text{m} \\ L &= 430 \text{ nH/m} \\ G &= 10 \text{ }\mu\text{S/m} \\ C &= 69 \text{ pF/m} \\ Z_0 &= 75 \text{ }\Omega \end{aligned}$$

**CAT5 Twisted Pair**



$$\begin{aligned} R &= 176 \text{ m}\Omega/\text{m} \\ L &= 490 \text{ nH/m} \\ G &= 2 \text{ }\mu\text{S/m} \\ C &= 49 \text{ pF/m} \\ Z_0 &= 100 \text{ }\Omega \end{aligned}$$


**Microstrip**

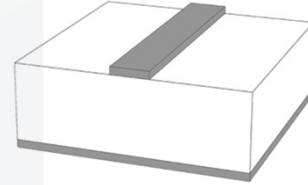


$$\begin{aligned} R &= 150 \text{ m}\Omega/\text{m} \\ L &= 364 \text{ nH/m} \\ G &= 3 \text{ }\mu\text{S/m} \\ C &= 107 \text{ pF/m} \\ Z_0 &= 50 \text{ }\Omega \end{aligned}$$

Surprisingly, almost all transmission lines have parameters very close to these values.

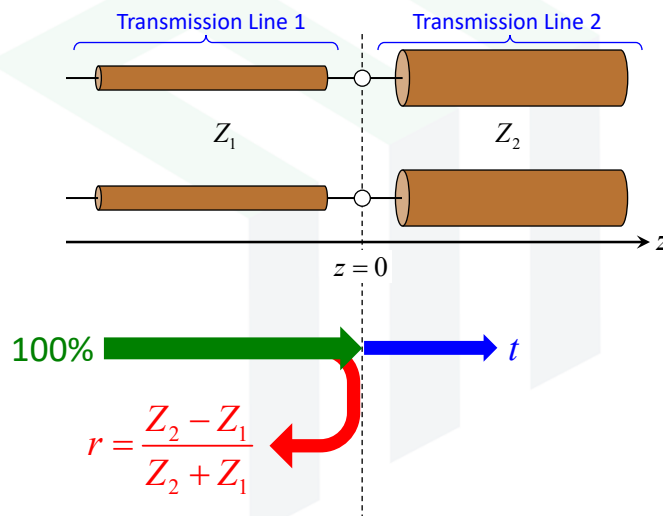
## Reflections From Impedance Discontinuities



# Voltage Standing Wave Ratio (VSWR)

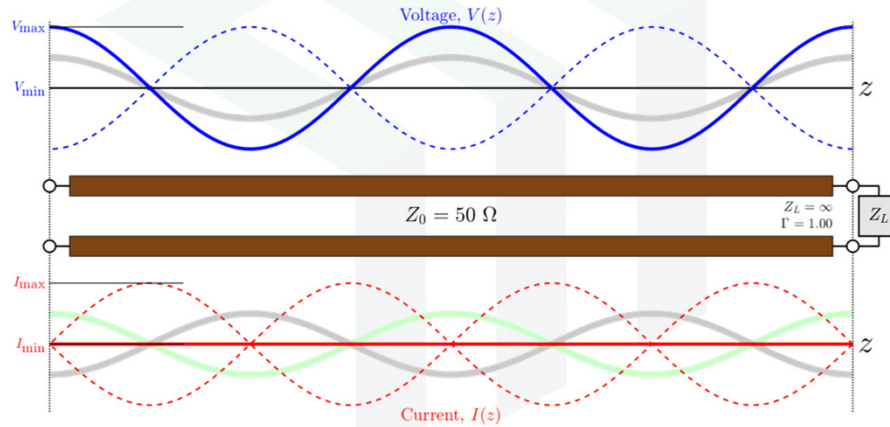

# Impedance Transformation

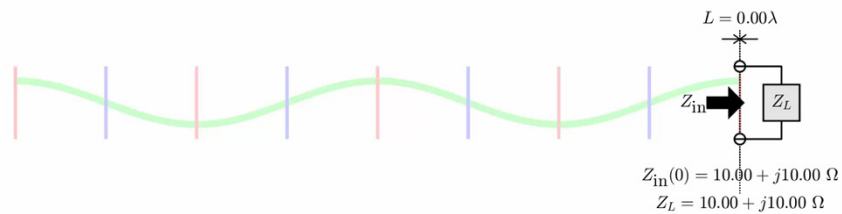


The impedance experienced by the source changes with distance away from the load!

Short circuits can look like open circuits, open circuits can look like short circuits, inductors can look like capacitors, capacitors can look like inductors,...its crazy!

$$Z_{in}(-\ell) = Z_0 \frac{Z_L + jZ_0 \tan(\beta\ell)}{Z_0 + jZ_L \tan(\beta\ell)}$$
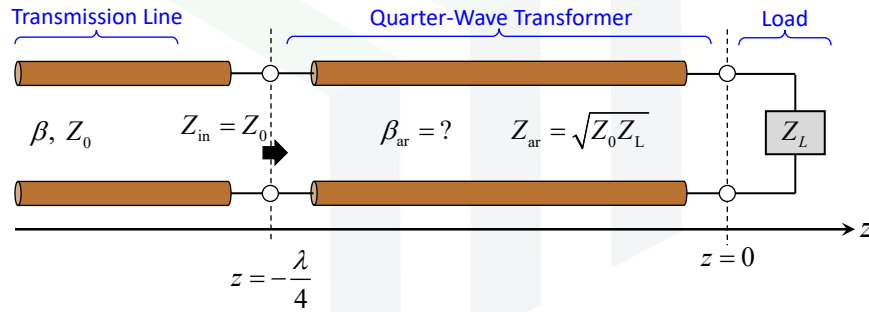
# Impedance Matching


A quarter-wavelength section of transmission line can be inserted between the main transmission and load to eliminate reflections.



An electromagnetic analysis of the transmission line must be performed in order to determine  $\beta_{ar}$ .

$$\ell = \frac{\lambda}{4} = \frac{\pi}{2\beta_{ar}}$$

# Multi-Segment Circuits

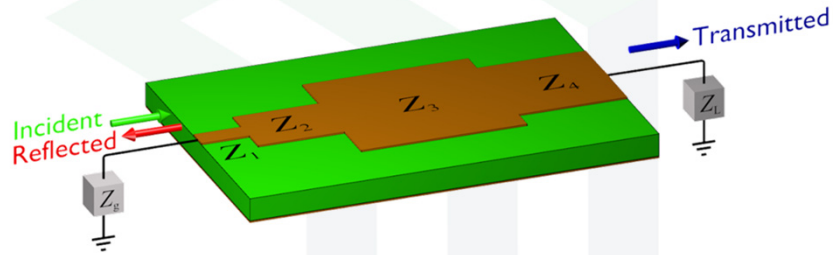

It becomes possible to design filters, pulse shapers, impedance matching circuits and much more.