



Electromagnetics:  
Microwave Engineering

# Transmission Line Resonators




## Lecture Outline

- Short-circuited  $\lambda/2$  resonator
- Short-circuited  $\lambda/4$  resonator
- Open-Circuited  $\lambda/2$  resonator


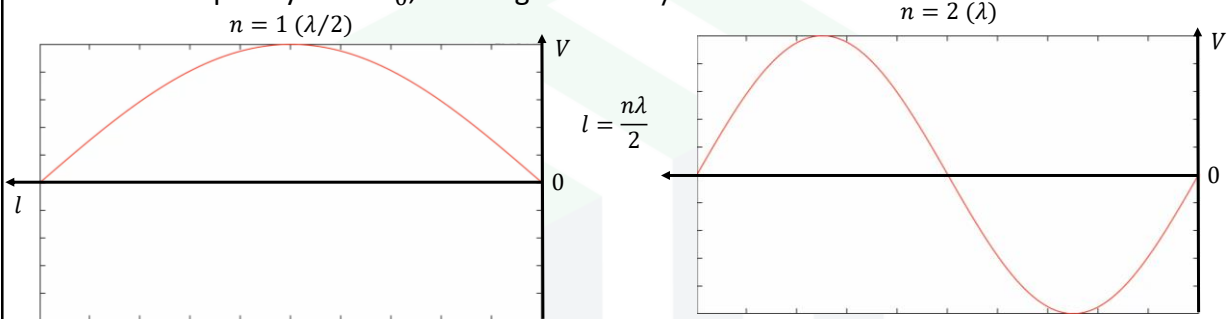
## Short-Circuited $\lambda/2$ Line Resonator

Resonant frequency  $\omega = \omega_0$ , the length is  $l = \lambda/2$



$$Z_{in} = Z_0 \tanh[(\alpha + j\beta)l]$$

$$Z_{in} = Z_0 \frac{\tanh(\alpha l) + j \tan(\beta l)}{1 + j \tan(\beta l) \tanh(\alpha l)}$$

For a low-loss transmission line,  $\alpha l \ll 1 \rightarrow \tan(\alpha l) \cong \alpha l$



## Short-Circuited $\lambda/2$ Line Resonator

For frequencies near resonance,  $\omega = \omega_0 + \Delta\omega$

$$\beta l = \frac{\omega l}{v_p} = \frac{\omega_0 l}{v_p} + \frac{\Delta\omega l}{v_p}$$

At the resonant frequency  $\omega = \omega_0$ , we have

$$l = \frac{\lambda}{2} = \pi \frac{v_p}{\omega_0}$$

$$\beta l = \pi + \frac{\Delta\omega \pi}{\omega_0}$$

$$\tan(\beta l) = \tan\left(\pi + \frac{\Delta\omega \pi}{\omega_0}\right) \cong \frac{\Delta\omega \pi}{\omega_0}$$



## Short-Circuited $\lambda/2$ Line Resonator

Using this result, the input impedance  $Z_{in}$  is

$$Z_{in} \cong Z_0 \frac{\alpha l + j \left( \frac{\Delta\omega\pi}{\omega_0} \right)}{1 + j \left( \frac{\Delta\omega\pi}{\omega_0} \right) \alpha l} \cong Z_0 \left( \alpha l + j \frac{\Delta\omega\pi}{\omega_0} \right)$$

This has the form of the input impedance of a series RLC resonant circuit

$$Z_{in} = R + 2jL\Delta\omega$$



## Short-Circuited $\lambda/2$ Line Resonator

The RLC parameters are

$$R = Z_0 \alpha l$$

$$L = \frac{Z_0 \pi}{2\omega_0}$$

$$C = \frac{1}{\omega_0^2 L}$$


And the unloaded  $Q$  factor  $Q_0$  is

$$Q_0 = \frac{\omega_0 L}{R} = \frac{\pi}{2\alpha l} = \frac{\beta}{2\alpha}$$


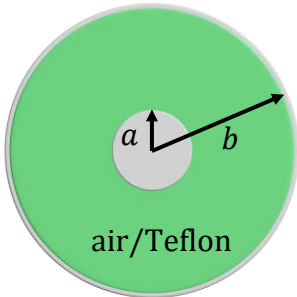
## Q of $\lambda/2$ Coaxial Line Resonator

Assume a  $\lambda/2$  resonator is made from a piece of copper coaxial line having an inner conductor radius of 1 mm and an outer conductor radius of 4 mm. If the resonant frequency is 5 GHz, compare the  $Q_0$  of an air-filled coaxial line to that of a Teflon-filled coaxial line resonator.



$$\begin{array}{lll}
 a = 1 \text{ mm} & \text{For air:} & \text{For Teflon:} \\
 b = 4 \text{ mm} & \epsilon_r = 1 & \epsilon_r = 2.08 \\
 & \tan \delta = 0 & \tan \delta = 0.0004
 \end{array}$$

Answer: First we calculate the attenuation of the coaxial line.

$$\sigma_{copper} = 5.813 \times 10^7 \text{ S/m}$$

The surface resistivity at 5 GHz is


$$R_s = \sqrt{\frac{\omega\mu_0}{2\sigma_{copper}}} = 1.84 \times 10^{-2} \Omega$$


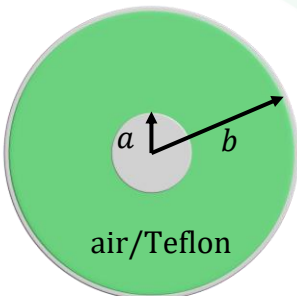
## Q of $\lambda/2$ Coaxial Line Resonator

The attenuation due to conductor loss is given by

$$\alpha_c = \frac{R_s}{2\eta \ln(b/a)} \left( \frac{1}{a} + \frac{1}{b} \right)$$



For air, the attenuation is

$$\alpha_{c,air} = \frac{R_s}{2(377) \ln(0.004/0.001)} \left( \frac{1}{0.001} + \frac{1}{0.004} \right) = 0.022 \text{ Np/m}$$

For Teflon, the attenuation is


$$\alpha_{c,Teflon} = \frac{R_s (\sqrt{2.08})}{2(377) \ln(0.004/0.001)} \left( \frac{1}{0.001} + \frac{1}{0.004} \right) = 0.032 \text{ Np/m}$$


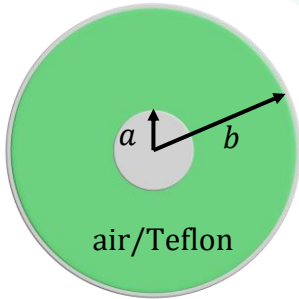
## Q of $\lambda/2$ Coaxial Line Resonator

Now we will calculate the attenuation due to dielectric loss

$$\alpha_d = k_0 \frac{\sqrt{\epsilon_r}}{2} \tan \delta$$



For air, since  $\tan \delta = 0$ , we have  $\alpha_d = 0$


For Teflon, the attenuation due to dielectric loss is

$$\alpha_d = \frac{2\pi \sqrt{\epsilon_r}}{\lambda_0} \tan \delta = \frac{(104.7)\sqrt{2.08} (0.0004)}{2} = 0.030 \text{ Np/m}$$



## Q of $\lambda/2$ Coaxial Line Resonator

We can calculate the unloaded Qs

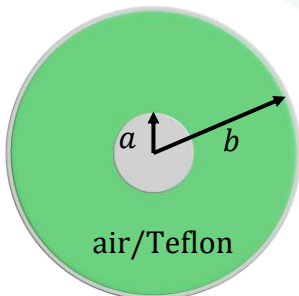

$$Q_{air} = \frac{\beta}{2\alpha} = \frac{104.7}{2(0.022)} = 2380$$

$$Q_{Teflon} = \frac{\beta}{2\alpha} = \frac{104.7}{2(0.032 + 0.030)} = 1218$$



## Short-Circuited $\lambda/4$ Line Resonator

Creates a parallel resonance (antiresonance). The input impedance is

$$\begin{aligned} Z_{in} &= Z_0 \tanh[(\alpha + j\beta)l] = Z_0 \frac{\tanh(\alpha l) + j \tan(\beta l)}{1 + j \tan(\beta l) \tanh(\alpha l)} \\ &= Z_0 \frac{1 - j \tanh(\alpha l) \cot(\beta l)}{\tanh(\alpha l) - j \cot(\beta l)} \end{aligned}$$

For the  $\lambda/4$  resonator, and at frequencies near resonance, we have

$$\begin{aligned} \beta l &= \frac{\omega_0 l}{v_p} + \frac{\Delta\omega l}{v_p} = \frac{\pi}{2} + \frac{\pi\Delta\omega}{2\omega_0} \\ \cot(\beta l) &\cong -\tan\left(\frac{\pi\Delta\omega}{2\omega_0}\right) \cong -\frac{\pi\Delta\omega}{2\omega_0} \end{aligned}$$



## Short-Circuited $\lambda/4$ Line Resonator

Assuming small loss,  $\tanh(\alpha l) \cong \alpha l$ , so  $Z_{in}$  is

$$Z_{in} = Z_0 \frac{1 + j\alpha l \pi \Delta\omega / 2\omega_0}{\alpha l + j\pi \Delta\omega / 2\omega_0} = \frac{Z_0}{\alpha l + j\pi \Delta\omega / 2\omega_0}$$

Which has the same form as the impedance of a parallel  $RLC$  circuit

$$Z_{in} = \frac{1}{(1/R) + 2j\Delta\omega C}$$

And the  $RLC$  parameters are

$$R = \frac{Z_0}{\alpha l} \quad L = \frac{1}{\omega_0^2 C} \quad C = \frac{\pi}{4\omega_0 Z_0}$$

And unloaded  $Q$  is given by


$$Q_0 = \omega_0 RC = \frac{\pi}{4\alpha l} = \frac{\beta}{2\alpha}$$


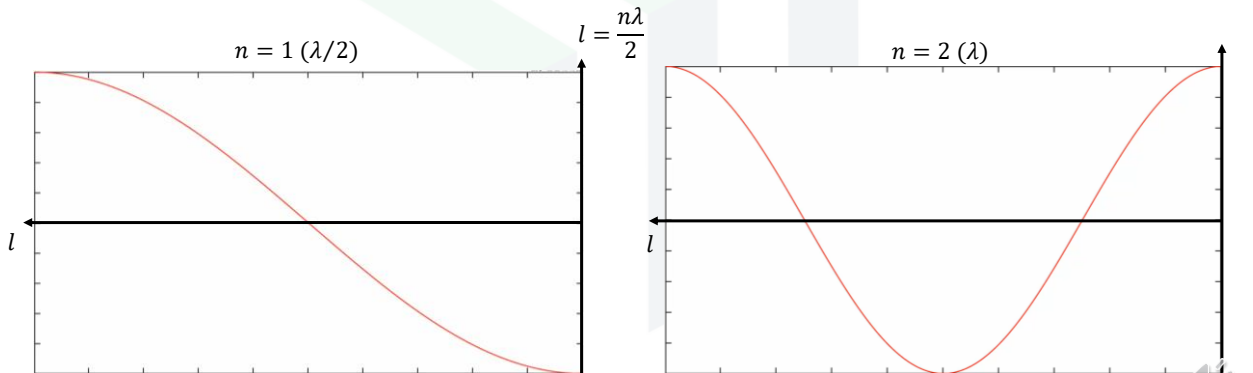
## Open-Circuited $\lambda/2$ Line Resonator

This resonator behaves as a parallel resonant circuit at multiples of  $\lambda/2$

$$Z_{in} = Z_0 \coth[(\alpha + j\beta)l] = Z_0 \frac{1 + j \tan(\beta l) \tanh(\alpha l)}{\tanh(\alpha l) + j \tan(\beta l)}$$



## Open-Circuited $\lambda/2$ Line Resonator

Assume  $l = \lambda/2$  at  $\omega = \omega_0$ , and let  $\omega = \omega_0 + \Delta\omega$

$$\beta l = \pi + \frac{\pi\Delta\omega}{\omega_0} \rightarrow \tan(\beta l) = \tan\left(\frac{\Delta\omega\pi}{\omega_0}\right) \cong \frac{\Delta\omega\pi}{\omega_0}, \quad \tan(\alpha l) \cong \alpha l$$

So the input impedance  $Z_{in}$  has the same form as a parallel resonant circuit

$$Z_{in} = \frac{Z_0}{\alpha l + j (\Delta\omega\pi/\omega_0)}$$

## Open-Circuited $\lambda/2$ Line Resonator

And the  $RLC$  parameters are

$$R = \frac{Z_0}{\alpha l}$$

$$L = \frac{1}{\omega_0^2 C}$$

$$C = \frac{\pi}{2\omega_0 Z_0}$$


And unloaded  $Q$  is given by

$$Q_0 = \frac{\pi}{2\alpha l} = \frac{\beta}{2\alpha}$$


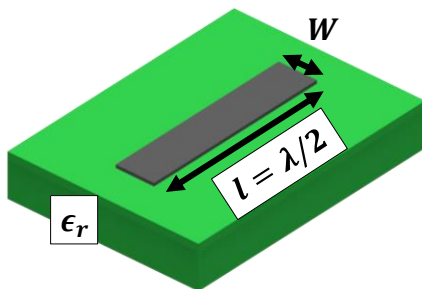
## $Q_0$ of Open-Circuited $\lambda/2$ Line Resonator

A microstrip resonator is constructed from a  $\lambda/2$  length of  $50 \Omega$  open-circuited microstrip line made of copper. The substrate is Teflon ( $\epsilon_r = 2.08$ ,  $\tan \delta = 0.0004$ ), with a thickness of  $0.159$  cm. Calculate the required length for resonance at  $5$  GHz and the unloaded  $Q$  of the resonator. Ignore fringing fields at the edge of the line.



Solution:

From Lecture 2c, "Transmission Line Examples", the width is

$$W = 0.508 \text{ cm}$$


And the effective permittivity is

$$\epsilon_{r,eff} = 1.80$$




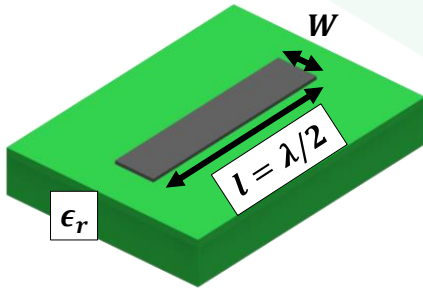
## $Q_0$ of Open-Circuited $\lambda/2$ Line Resonator



The resonant length can now be calculated:


$$l = \frac{\lambda}{2} = \frac{c_0}{2f \sqrt{\epsilon_{r,eff}}} = 2.24 \text{ cm}$$

The propagation constant  $\beta$  is

$$\beta = \frac{2\pi f}{v_p} = \frac{2\pi f \sqrt{\epsilon_{r,eff}}}{c_0} = 151.0 \text{ rad/m}$$


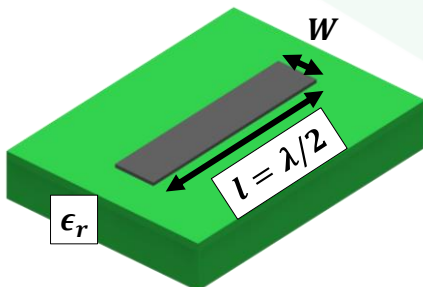
## $Q_0$ of Open-Circuited $\lambda/2$ Line Resonator



The attenuation due to conductor loss in a microstrip line is

$$\alpha_c = \frac{R_s}{Z_0 W} = \frac{1.84 \times 10^{-2}}{50(0.00508)} = 0.0724 \text{ Np/m}$$

The attenuation due to the dielectric loss in a microstrip is

$$\alpha_d = \frac{k_0 \epsilon_r (\epsilon_{r,eff} - 1) \tan \delta}{2 \sqrt{\epsilon_{r,eff}} (\epsilon_r - 1)} = 0.024 \text{ Np/m}$$

And the unloaded  $Q$  is

$$Q = \frac{\beta}{2\alpha} = \frac{151.0}{2(0.0724 + 0.024)} = 783$$

