



Electromagnetics:
Microwave Engineering

Power Dividers and Directional Couplers



Slide 1


Lecture Outline

- Basic Properties of Dividers and Couplers
- Three-Port Networks
- Four-Port Networks
- Characterization of Directional Couplers
- Hybrid Couplers



2

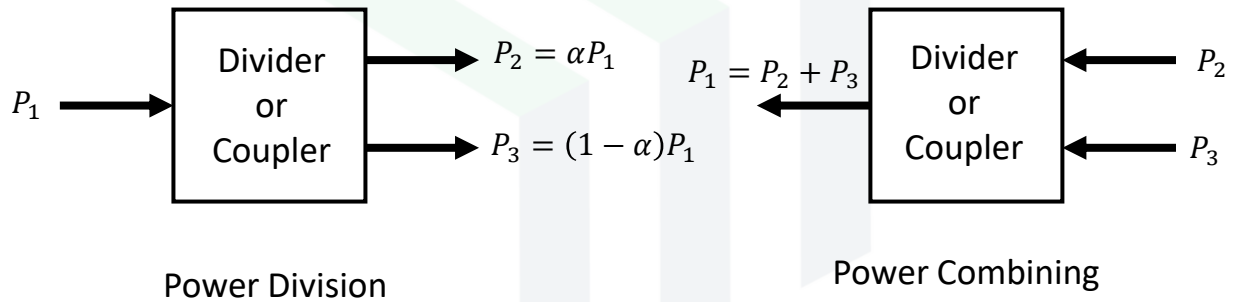Basic Properties of Dividers and Couplers



Three-Port Networks

The simplest type of power divider is the *T-junction*, a three-port network with two inputs and one output

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix}$$

If the device is passive and isotropic, it must be reciprocal and symmetric ($S_{ij} = S_{ji}$). It is desired to have a junction that is lossless and matched ($S_{ii} = 0$). If the network is reciprocal and matched, we obtain

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{21} & 0 & S_{23} \\ S_{31} & S_{32} & 0 \end{bmatrix}$$



Three-Port Networks

For a network to be lossless, we have the following conditions:

$$|S_{12}|^2 + |S_{13}|^2 = 1$$

$$S_{13}^* S_{23} = 0$$

$$|S_{12}|^2 + |S_{23}|^2 = 1$$

$$S_{23}^* S_{12} = 0$$

$$|S_{13}|^2 + |S_{23}|^2 = 1$$

$$S_{12}^* S_{13} = 0$$

It is impossible to satisfy all of these conditions, so a three-port network cannot be reciprocal, lossless, and matched at all ports. One of these conditions must be relaxed.



Three-Port Networks

We can have a matched, lossless, non-reciprocal three-port network.

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{21} & 0 & S_{23} \\ S_{31} & S_{32} & 0 \end{bmatrix}$$

For a lossless network, $[S]$ is unitary, and the following conditions apply:

$$|S_{12}|^2 + |S_{13}|^2 = 1$$

$$S_{31}^* S_{32} = 0$$

$$|S_{21}|^2 + |S_{23}|^2 = 1$$

$$S_{21}^* S_{23} = 0$$

$$|S_{31}|^2 + |S_{32}|^2 = 1$$

$$S_{12}^* S_{13} = 0$$



Three-Port Networks

The previous equations can be satisfied in two ways:


a. $S_{12} = S_{23} = S_{31} = 0, \quad |S_{21}| = |S_{32}| = |S_{13}| = 1$

b. $S_{21} = S_{32} = S_{13} = 0, \quad |S_{12}| = |S_{23}| = |S_{31}| = 1$

The two cases lead to two possible types of circulators:


a.
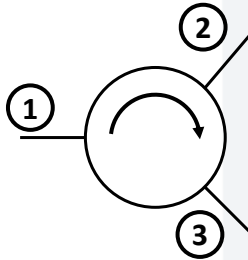
$$[S] = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$



b.
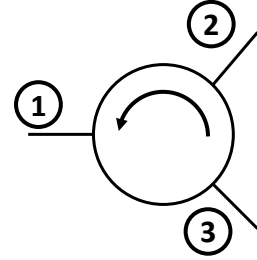
$$[S] = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{bmatrix}$$



Four-Port Networks (Directional Couplers)

The scattering matrix of a reciprocal four-port network matched at all ports has the form:

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & S_{14} \\ S_{12} & 0 & S_{23} & S_{24} \\ S_{13} & S_{23} & 0 & S_{34} \\ S_{14} & S_{24} & S_{34} & 0 \end{bmatrix}$$

For a reciprocal and lossless network, the following conditions apply:

$$\sum_{k=1}^N S_{ki} S_{ki}^* = 1$$

$$\sum_{k=1}^N S_{ki} S_{kj}^* = 0, \quad i \neq j$$



Four-Port Networks (Directional Couplers)

Which leads to a series of 10 equations:

$$\boxed{1} \quad |S_{12}|^2 + |S_{13}|^2 + |S_{14}|^2 = 1$$

$$\boxed{2} \quad |S_{12}|^2 + |S_{23}|^2 + |S_{24}|^2 = 1$$

$$\boxed{3} \quad |S_{13}|^2 + |S_{23}|^2 + |S_{34}|^2 = 1$$

$$\boxed{4} \quad |S_{14}|^2 + |S_{24}|^2 + |S_{34}|^2 = 1$$

$$\boxed{5} \quad S_{13}^* S_{23} + S_{14}^* S_{24} = 0$$

$$\boxed{6} \quad S_{12}^* S_{23} + S_{14}^* S_{34} = 0$$

$$\boxed{7} \quad S_{24}^* S_{12} + S_{34}^* S_{13} = 0$$

$$\boxed{8} \quad S_{13}^* S_{12} + S_{34}^* S_{24} = 0$$

$$\boxed{9} \quad S_{14}^* S_{12} + S_{34}^* S_{23} = 0$$

$$\boxed{10} \quad S_{14}^* S_{13} + S_{24}^* S_{23} = 0$$

Four-Port Networks (Directional Couplers)

We multiply eq. $\boxed{5}$ by S_{24}^* , and eq. $\boxed{10}$ by S_{13}^*

$$S_{24}^* (S_{13} S_{23}^* + S_{14} S_{24}^*) = 0$$

$$S_{13}^* (S_{13} S_{14}^* + S_{23} S_{24}^*) = 0$$

We subtract the equations to obtain

$$S_{14}^* (|S_{13}|^2 + |S_{24}|^2) = 0$$

Similarly, we multiply eq. $\boxed{6}$ by S_{12} and eq. $\boxed{9}$ by S_{34}

$$S_{12} (S_{12}^* S_{23} + S_{14}^* S_{34}) = 0$$

$$S_{34} (S_{14}^* S_{12} + S_{34}^* S_{23}) = 0$$

We subtract the equations to obtain

$$S_{23} (|S_{12}|^2 + |S_{34}|^2) = 0$$

Four-Port Networks (Directional Couplers)

The pair of equations

$$S_{14}^*(|S_{13}|^2 + |S_{24}|^2) = 0$$

$$S_{23}(|S_{12}|^2 + |S_{34}|^2) = 0$$

can be satisfied if $S_{14} = S_{23} = 0$

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & 0 \\ S_{12} & 0 & 0 & S_{24} \\ S_{13} & 0 & 0 & S_{34} \\ 0 & S_{24} & S_{34} & 0 \end{bmatrix}$$

These conditions imply that there is no coupling between ports 1 and 4 and between ports 2 and 3, which results in a directional coupler.

Four-Port Networks (Directional Couplers)

Now the set of 10 equations reduce to

$$\boxed{1} \quad |S_{12}|^2 + |S_{13}|^2 = 1$$

$$\boxed{2} \quad |S_{12}|^2 + |S_{24}|^2 = 1$$

$$\boxed{3} \quad |S_{13}|^2 + |S_{34}|^2 = 1$$

$$\boxed{4} \quad |S_{24}|^2 + |S_{34}|^2 = 1$$

$$\boxed{5} \quad S_{12}^* S_{24} + S_{13}^* S_{34} = 0$$

$$\boxed{6} \quad S_{12}^* S_{13} + S_{24}^* S_{34} = 0$$

Eqs. $\boxed{1}$ and $\boxed{2}$ imply that $|S_{13}| = |S_{24}|$, and eqs. $\boxed{2}$ and $\boxed{4}$ imply that $|S_{12}| = |S_{34}|$

Four-Port Networks (Directional Couplers)

We can simplify more by choosing the phase references on three of the four ports

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & 0 \\ S_{12} & 0 & 0 & S_{24} \\ S_{13} & 0 & 0 & S_{34} \\ 0 & S_{24} & S_{34} & 0 \end{bmatrix}$$

$$\begin{aligned} S_{12} &= S_{34} = \alpha \\ S_{13} &= \beta e^{j\theta} \\ S_{24} &= \beta e^{j\phi} \end{aligned}$$

Where α and β are real, θ and ϕ are phase constants to be determined. Eq. 6 leads to

$$S_{12}^* S_{13} + S_{24}^* S_{34} = 0 \quad \longrightarrow \quad \theta + \phi = \pi + 2n\pi$$

By letting $n = 0$, we have two choices of couplers.

Four-Port Networks (Directional Couplers)

1. *Symmetric Coupler* ($\theta = \phi = \pi/2$)

$$[S] = \begin{bmatrix} 0 & \alpha & j\beta & 0 \\ \alpha & 0 & 0 & j\beta \\ j\beta & 0 & 0 & \alpha \\ 0 & j\beta & \alpha & 0 \end{bmatrix}$$


2. *Antisymmetric Coupler* ($\theta = 0, \phi = \pi$)

$$[S] = \begin{bmatrix} 0 & \alpha & \beta & 0 \\ \alpha & 0 & 0 & -\beta \\ \beta & 0 & 0 & \alpha \\ 0 & -\beta & \alpha & 0 \end{bmatrix}$$

These two couplers differ only in the choice of reference planes, and eq. 1 requires that

$$\alpha^2 + \beta^2 = 1$$

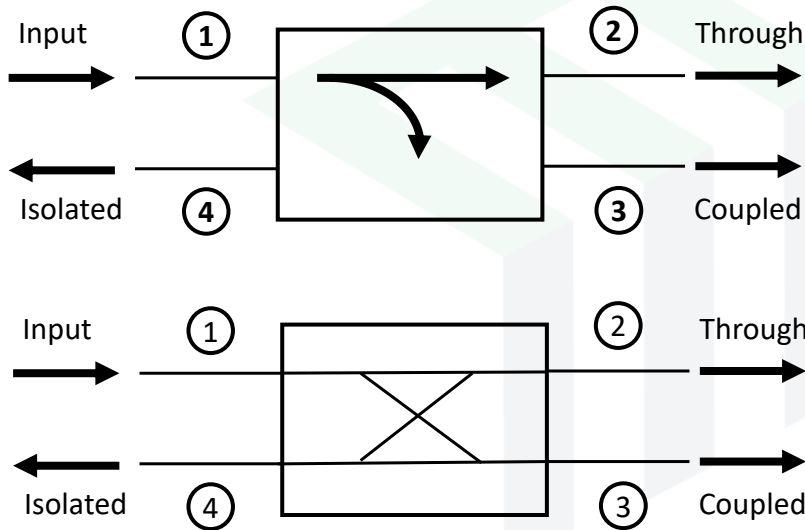Four-Port Networks (Directional Couplers)



- Power supplied to Port 1 is coupled to Port 3
 $|S_{13}|^2 = \beta^2$
- The remainder of the input power is delivered to Port 2
 $|S_{12}|^2 = \alpha^2 = 1 - \beta^2$
- Ideally, no power is delivered to Port 4

Characterization of Directional Couplers

- Coupling C
 $C = 10 \log \left(\frac{P_1}{P_3} \right) = -20 \log(\beta) \text{ dB}$
 C – The fraction of the input power that is coupled to the output port
- Directivity D
 $D = 10 \log \left(\frac{P_3}{P_4} \right) = 20 \log \left(\frac{\beta}{|S_{14}|} \right) \text{ dB}$
 D – Coupler's ability to isolate coupled and uncoupled ports
- Isolation I
 $I = 10 \log \left(\frac{P_1}{P_4} \right) = -20 \log(|S_{14}|) \text{ dB}$
 I – Power delivered to the uncoupled port ($I = D + C$)
- Insertion Loss L
 $L = 10 \log \left(\frac{P_1}{P_2} \right) = -20 \log(|S_{12}|) \text{ dB}$
 L – Input power delivered to the through port, diminished by power delivered to the coupled and isolated ports

Note: for ideal couplers, $S_{14} = 0, D = \infty$

Hybrid Couplers

Hybrid Couplers are a special type of couplers where the coupling factor C is 3 dB

$$(\alpha = \beta = 1/\sqrt{2})$$

- Quadrature Hybrid: A symmetric coupler that has a 90° phase shift between ports 2 and 3 ($\theta = \phi = \pi/2$) when fed at port 1

$$[S] = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & j & 0 \\ 1 & 0 & 0 & j \\ j & 0 & 0 & 1 \\ 0 & j & 1 & 0 \end{bmatrix}$$

- Magic-T and Rat-Race: An antisymmetric coupler that has a 180° phase shift between ports 2 and 3 when fed at port 4

$$[S] = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}$$