



Electromagnetics:  
Microwave Engineering

# The Wilkinson Power Divider



Slide 1

## Lecture Outline

- Basic Properties of Wilkinson Power Dividers
- Normalized and Symmetric Wilkinson Power Divider
- Even-Mode Analysis
- Odd-Mode Analysis
- Scattering Parameters for Wilkinson Power Divider
- Unequal Power Division in Wilkinson Divider
- Example – Design of a Wilkinson Power Divider




2

# Basic Properties of Wilkinson Power Dividers

- The Wilkinson Power Divider is a lossy three-port network that has all port matched, and the ports are isolated
- The Wilkinson Power Divider was developed by Ernest J. Wilkinson in 1960
- It splits an input signal into two equal output signals in phase
- It can combine two inputs constructively to a single output
- If the output ports are matched, the Wilkinson Power Divider will appear lossless

# Basic Properties of Wilkinson Power Dividers


## Equal-Split Wilkinson Power Divider

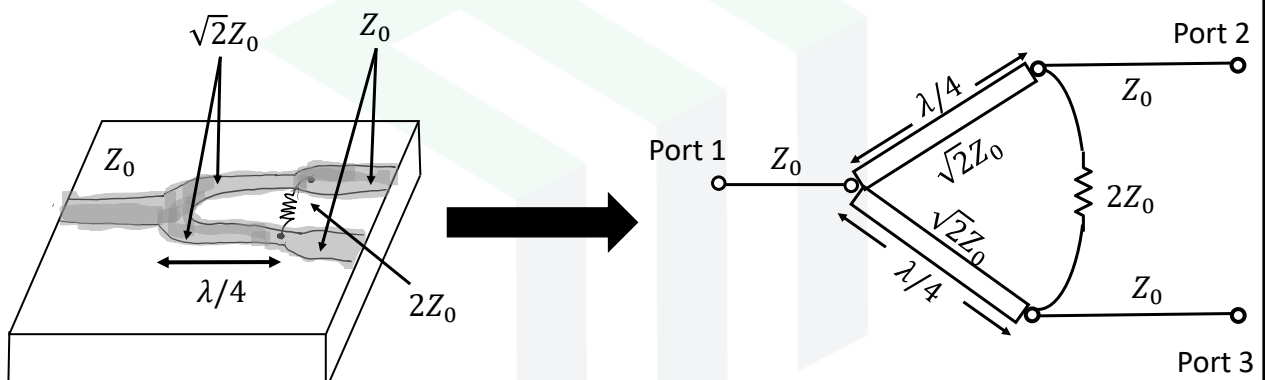

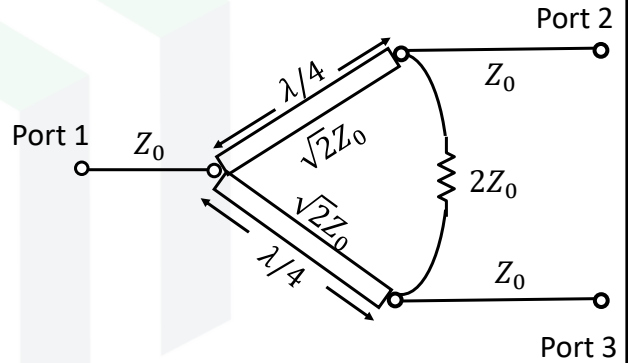
# Basic Properties of Wilkinson Power Dividers

How to obtain S-parameters of the Wilkinson Power Divider?

- Taking advantage of the symmetry of the circuit, we can redraw the power divider in normalized and symmetric form.
- This will allow to analyze the circuit by simplifying to two simpler circuits driven by symmetric and antisymmetric sources (Even- and Odd-Mode Analysis).
- All impedances will be normalized to the characteristic impedance  $Z_0$ .



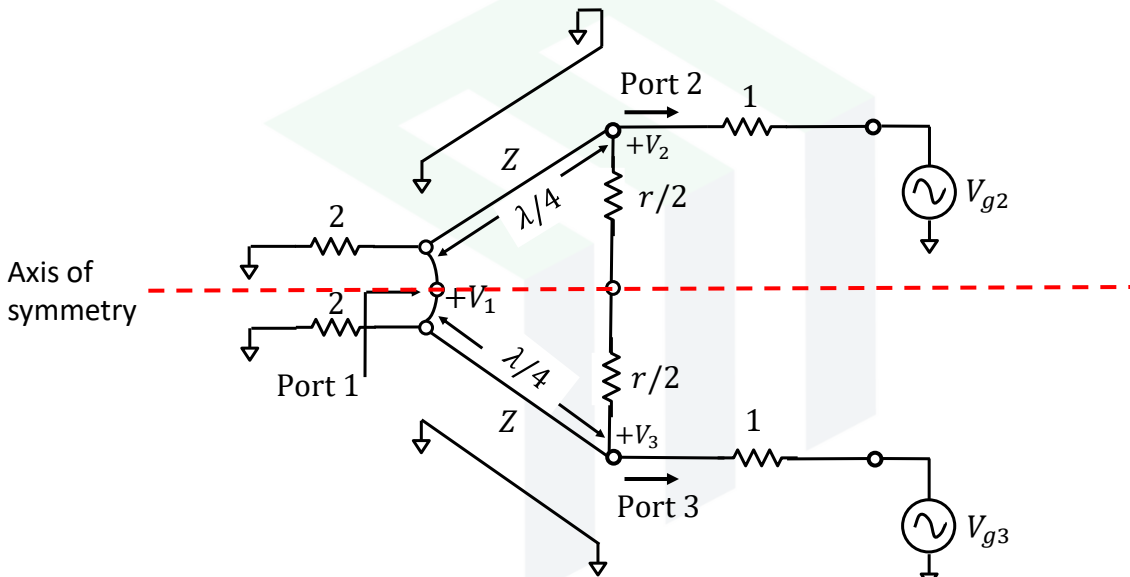
# Normalized and Symmetric Wilkinson Power Divider



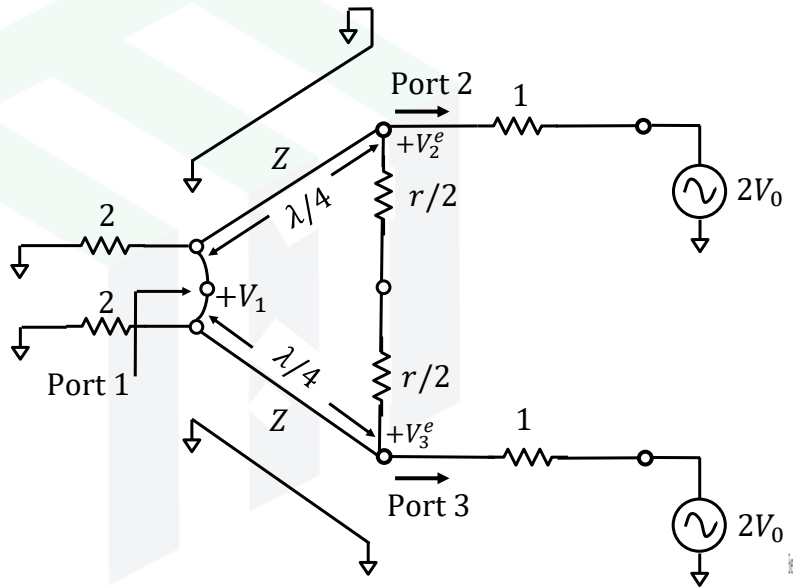
## Even-Mode Analysis ( $V_{g2} = V_{g3} = 2V_0$ )

- $V_2^e = V_3^e$
- No current goes through  $r/2$  resistors
- The circuit can be separated at the middle and replace the bisections with open circuits


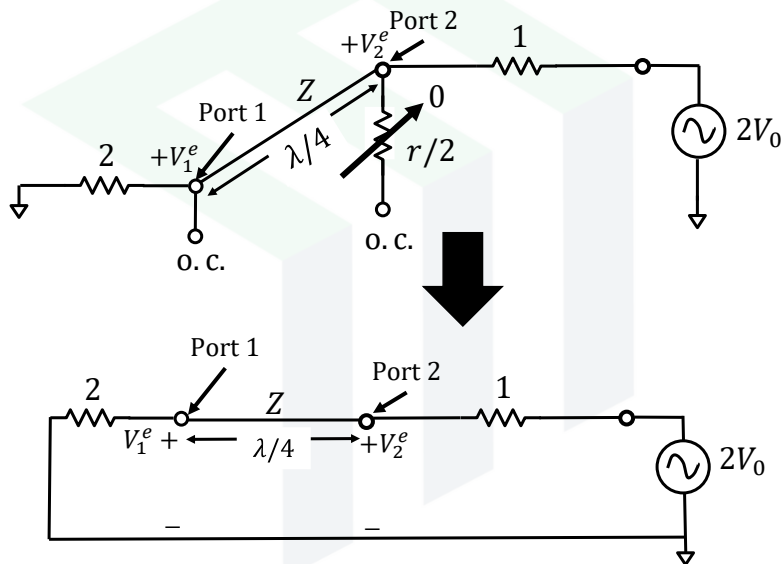
## Even-Mode Analysis ( $V_{g2} = V_{g3} = 2V_0$ )



## Even-Mode Analysis ( $V_{g2} = V_{g3} = 2V_0$ )

- The input impedance at Port 2 with the  $\lambda/4$  T.L. and the 2 resistor

$$Z_{in} \left( -\frac{\lambda}{4} \right) = \frac{Z^2}{Z_L} = \frac{Z^2}{2}$$

- For port 2 to be matched,

$$Z = \sqrt{2}$$



And  $Z_{in} = 1$

- Now we obtain

$$V_2^e = V_0$$

And by even symmetry,

$$V_3^e = V_0$$

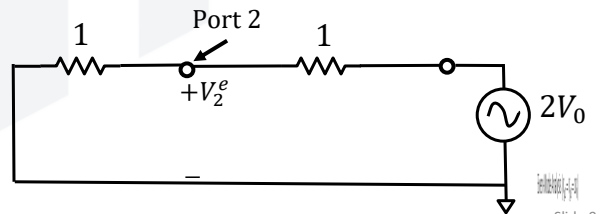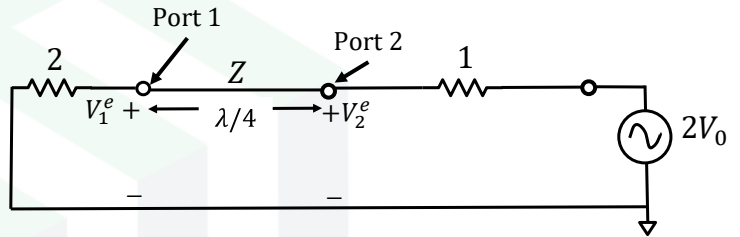

## Even-Mode Analysis ( $V_{g2} = V_{g3} = 2V_0$ )

- To find the voltage at Port 1,

$$x = 0 \text{ at Port 1}$$

$$x = -\lambda/4 \text{ at Port 2}$$

The expression for voltage is


$$V(x) = V^+(e^{-j\beta x} + \Gamma e^{j\beta x})$$

$$V_2^e = V(-\lambda/4) = jV^+(1 - \Gamma) = V_0$$

$$V_1^e = V(0) = V^+(1 + \Gamma) = jV_0 \frac{\Gamma + 1}{\Gamma - 1}$$


$$\Gamma = \frac{2 - \sqrt{2}}{2 + \sqrt{2}}$$

Then we obtain  $V_1^e = -jV_0\sqrt{2}$

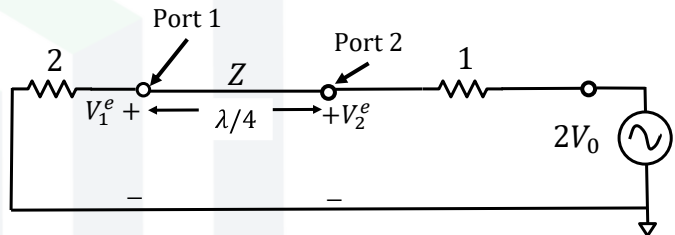
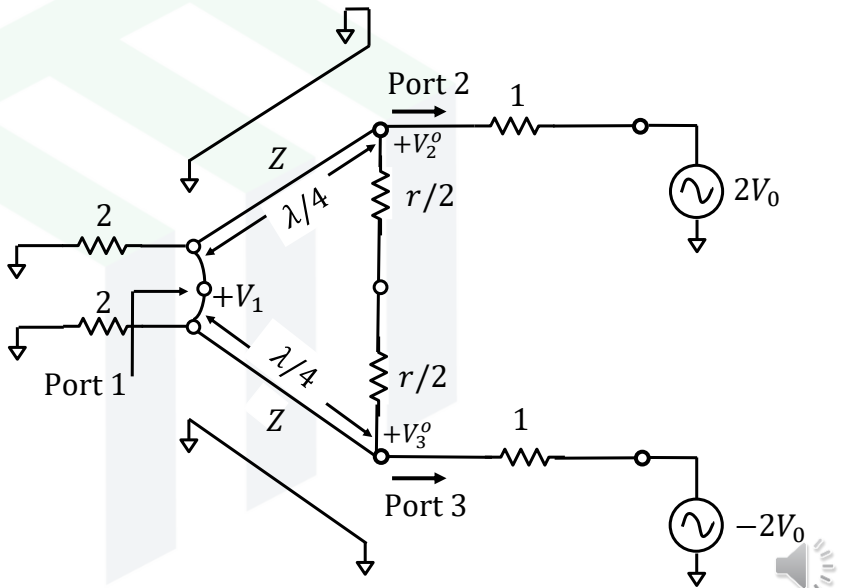
## Odd-Mode Analysis ( $V_{g2} = -V_{g3} = 2V_0$ )

- $V_2^o = -V_3^o$
- A voltage null is present along the middle of the circuit
- The circuit can be separated at the middle and replace the bisections with ground



## Odd-Mode Analysis ( $V_{g2} = -V_{g3} = 2V_0$ )

- The voltage at Port 2 is the voltage present at the  $r/2$  resistor
- To match Port 2 for odd-mode  $r = 2$ .
- We obtain


$$V_2^o = V_0$$

and by odd symmetry

$$V_3^o = -V_0$$

- Since Port 1 is short-circuited,

$$V_1^o = 0$$

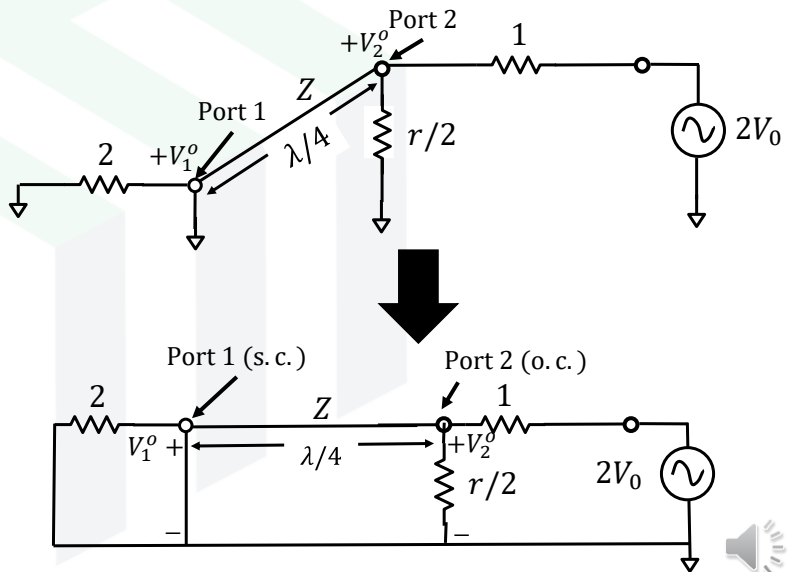

# Scattering Parameters for Wilkinson Power Divider

Now with superposition the total voltage can be obtained

Total Voltage at Port 1:

$$V_1^t = V_1^e + V_1^o = -jV_0\sqrt{2}$$


Total Voltage at Port 2:

$$V_2^t = V_2^e + V_2^o = 2V_0$$

Total Voltage at Port 3:

$$V_3^t = V_3^e + V_3^o = 0$$

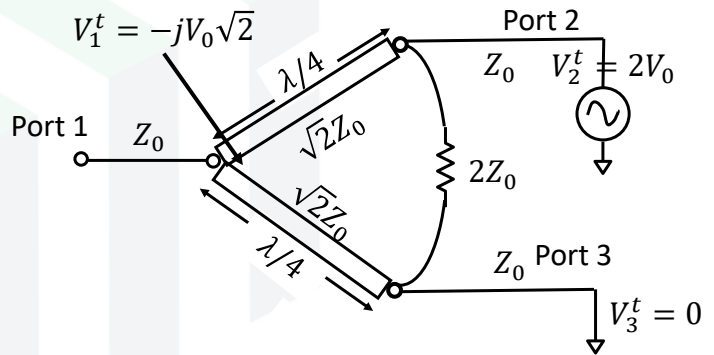The total voltages can correspond to a matched source  $2V_0$  at Port 2, and Ports 1 and 3 also matched.



# Scattering Parameters for Wilkinson Power Divider

The incident and reflected voltages are then

Ports	$V^+$	$V^-$
Port 1	$V_1^+ = 0$	$V_1^- = -jV_0\sqrt{2}$
Port 2	$V_2^+ = 2V_0$	$V_2^- = 0$
Port 3	$V_3^+ = 0$	$V_3^- = 0$

And the scattering parameters can be obtained:

$$S_{12} = \frac{V_1^-}{V_2^+} = \frac{-jV_0\sqrt{2}}{2V_0} = -\frac{j}{\sqrt{2}} = S_{21} \quad (\text{symmetry due to reciprocity})$$


$$S_{13} = S_{31} = -\frac{j}{\sqrt{2}} \quad (\text{symmetry of ports 2 and 3})$$

$$S_{23} = \frac{V_2^-}{V_3^+} = 0 = S_{32} \quad (\text{ports are isolated due to short or open circuit at bisection})$$

$$S_{22} = \frac{V_2^-}{V_2^+} = 0 = S_{33} \quad (\text{symmetry of ports 2 and 3})$$
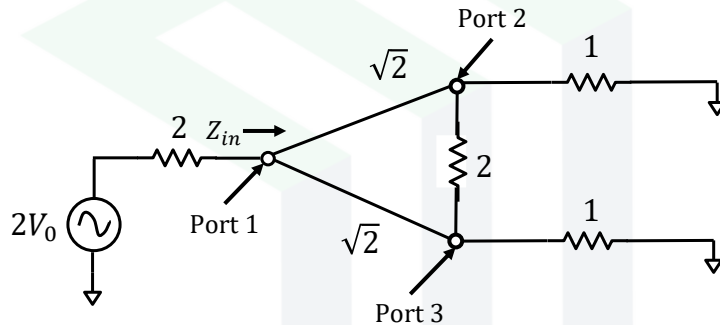
# Scattering Parameters for Wilkinson Power Divider

To find  $S_{11}$ , we drive Port 1 with voltage source  $2V_0$  with matched loads at Ports 2 and 3 and find the normalized input impedance  $Z_{in}$ :



The input impedance is then


$$Z_{in} = \frac{(\sqrt{2})^2}{2} = 1$$

# Scattering Parameters for Wilkinson Power Divider

Since  $Z_{in} = 1$ , the source is matched, and we have:

$$S_{11} = 0$$

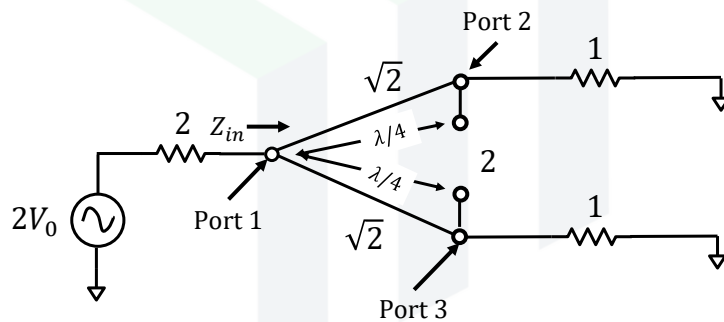Furthermore, the voltage is split equally and with the same phase at Ports 2 and 3, so no power is dissipated in the resistor, making the divider lossless when the outputs are matched.





# Scattering Parameters for Wilkinson Power Divider

Putting everything together, the scattering matrix for the Wilkinson Power Divider is:

$$[S] = \frac{-j}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 0 \\ 1 & 0 & 0 \end{bmatrix}$$

# Unequal Power Division in Wilkinson Divider


Wilkinson power dividers can also be made with unequal power splits. Considering the power ratio between ports 2 and 3,

$$K^2 = P_3/P_2$$

$$Z_{03} = Z_0 \sqrt{\frac{1 + K^2}{K^3}}$$

$$Z_{02} = K^2 Z_{03} = Z_0 \sqrt{K(1 + K^2)}$$
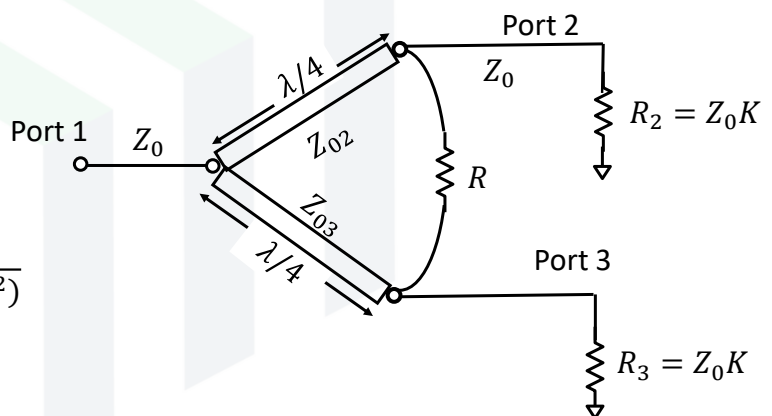
$$R = Z_0 \left( K + \frac{1}{K} \right)$$



## Example – Design of a Wilkinson Power Divider

Design an equal-split Wilkinson Power Divider for a  $50 \Omega$  system impedance at a frequency  $f_0$ .

Solution:

The quarter-wave transmission lines in the divider have a characteristic impedance of

$$Z = \sqrt{2}Z_0 = 70.7 \Omega$$

The shunt resistor value is

$$R = 2Z_0 = 100 \Omega$$

And the transmission lines are  $\lambda/4$  long at frequency  $f_0$