



Electromagnetics:
Microwave Engineering

The Quadrature (90°) Hybrid Directional Coupler



Slide 1

Lecture Outline


- Properties of the Quadrature (90°) Hybrid
- Normalized and Symmetric Form
- Even- and Odd- Mode Analysis
- Transmission and Reflection Coefficients
- Characteristics of Quadrature Hybrid Coupler
- Example – Design of a Quadrature Hybrid




2

Properties of the Quadrature (90°) Hybrid

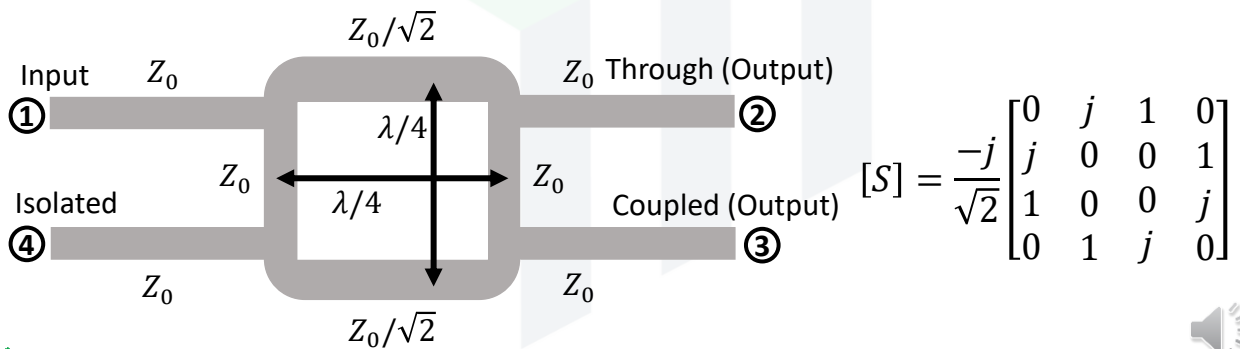
- The Quadrature Hybrid is a 3 dB directional coupler with a 90° phase difference in the outputs of the through and coupled arms.
- It is also called branch-line hybrid.
- Due to the high symmetry of the coupler, any port can be used as input port, and even-odd analysis can be performed



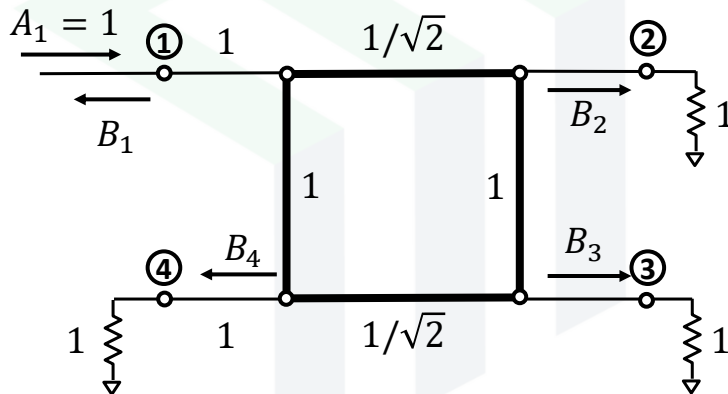
Normalized and symmetric form of Quadrature Hybrid




Even-Mode of Quadrature Hybrid

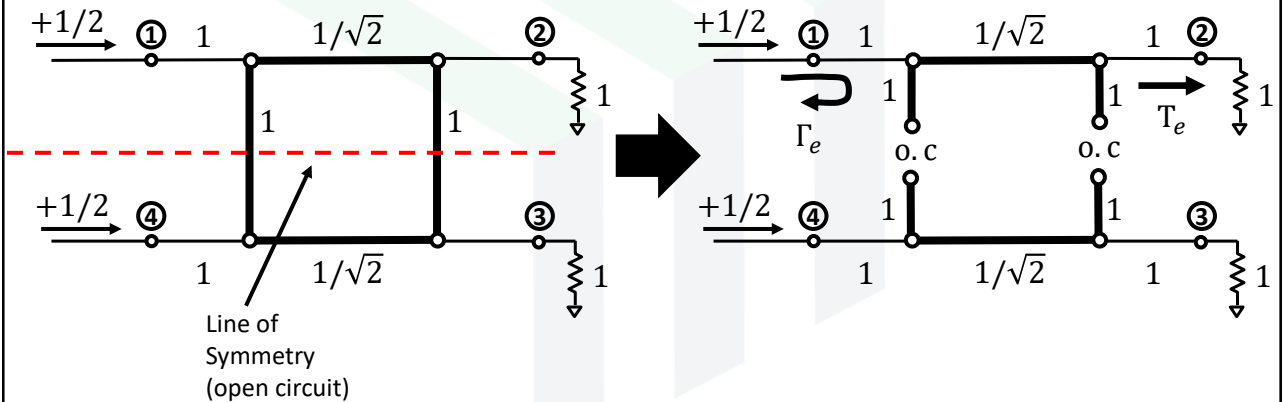

Odd-Mode of Quadrature Hybrid

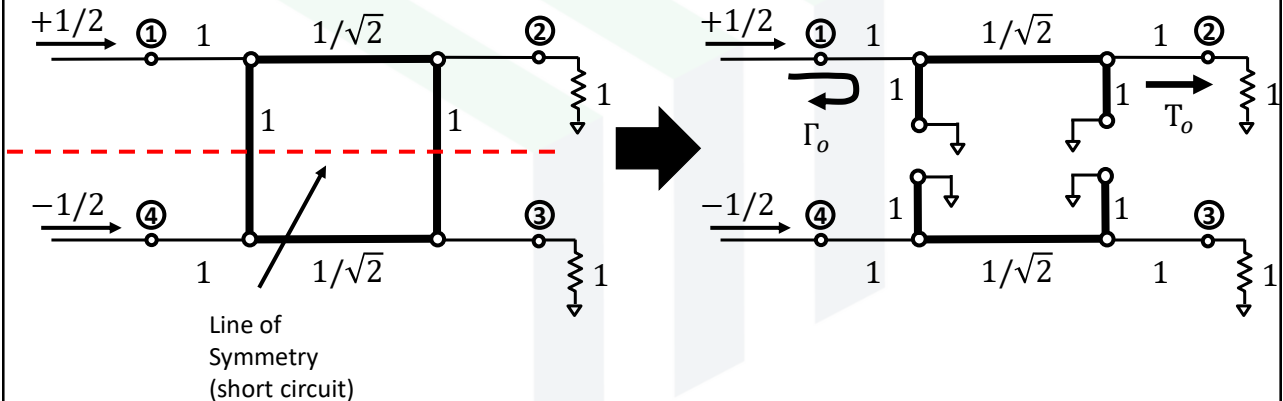

Even-Odd Mode of Quadrature Hybrid

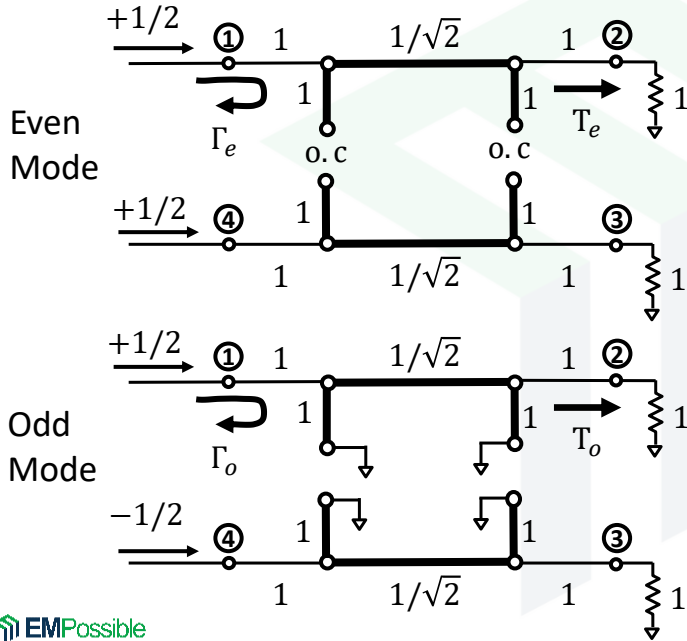


$$B_1 = \frac{1}{2}\Gamma_e + \frac{1}{2}\Gamma_o$$

$$B_2 = \frac{1}{2}T_e + \frac{1}{2}T_o$$

$$B_3 = \frac{1}{2}T_e - \frac{1}{2}T_o$$

$$B_4 = \frac{1}{2}\Gamma_e - \frac{1}{2}\Gamma_o$$

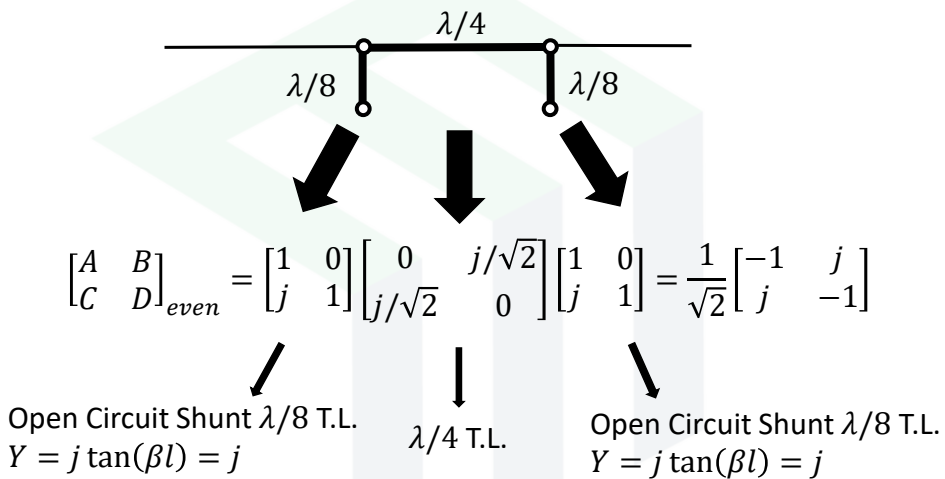Transmission and Reflection Coefficients – Even Mode




Transmission and Reflection Coefficients – Even Mode

$$\Gamma_e = \frac{A + B - C - D}{A + B + C + D} = \frac{(1 + j - j + 1)/\sqrt{2}}{(1 + j + j - 1)/\sqrt{2}} = 0$$

$$T_e = \frac{2}{A + B + C + D} = \frac{2}{(1 + j + j - 1)/\sqrt{2}} = -\frac{1}{\sqrt{2}}(1 + j)$$

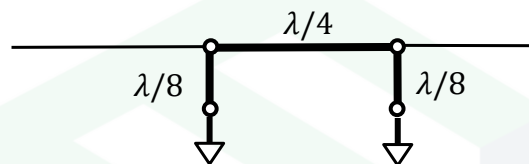Transmission and Reflection Coefficients - Odd Mode



$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_{odd} = \begin{bmatrix} 1 & 0 \\ -j & 1 \end{bmatrix} \begin{bmatrix} 0 & j/\sqrt{2} \\ j/\sqrt{2} & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ -j & 1 \end{bmatrix} = \frac{1}{\sqrt{2}} \begin{bmatrix} 1 & j \\ j & 1 \end{bmatrix}$$

Short-Circuit Shunt $\lambda/8$ T.L.
 $Y = -j \cot(\beta l) = -j$

$\lambda/4$ T.L.

Short-Circuit Shunt $\lambda/8$ T.L.
 $Y = -j \cot(\beta l) = -j$

Transmission and Reflection Coefficients – Odd Mode

$$\Gamma_o = \frac{A + B - C - D}{A + B + C + D} = \frac{(1 + j - j - 1)/\sqrt{2}}{(1 + j + j + 1)/\sqrt{2}} = 0$$

$$T_o = \frac{2}{A + B + C + D} = \frac{2}{(1 + j + j + 1)/\sqrt{2}} = \frac{1}{\sqrt{2}}(1 - j)$$

Characteristics of Quadrature Hybrid Coupler

$$B_1 = \frac{1}{2}(0) + \frac{1}{2}(0) = 0$$

Port 1 is matched

$$B_2 = \frac{1}{2}\left(-\frac{1}{\sqrt{2}} - \frac{j}{\sqrt{2}}\right) + \frac{1}{2}\left(\frac{1}{\sqrt{2}} - \frac{j}{\sqrt{2}}\right) = -\frac{j}{\sqrt{2}}$$

Half of power with -90° phase shift is transmitted from Port 1 to Port 2

$$B_3 = \frac{1}{2}\left(-\frac{1}{\sqrt{2}} - \frac{j}{\sqrt{2}}\right) - \frac{1}{2}\left(\frac{1}{\sqrt{2}} - \frac{j}{\sqrt{2}}\right) = -\frac{1}{\sqrt{2}}$$

Half of power with -180° phase shift is transmitted from Port 1 to Port 3

$$B_4 = \frac{1}{2}(0) - \frac{1}{2}(0) = 0$$

No power to Port 4 (isolated)

Example – Design of a Quadrature Hybrid

Design a $50\ \Omega$ branch-line quadrature hybrid junction at a frequency f_0 .

Solution:

The transmission lines will be $\lambda/4$ long at the design frequency f_0 . The branch-line impedances are

$$\frac{Z_0}{\sqrt{2}} = \frac{50}{\sqrt{2}} = 35.4\ \Omega$$