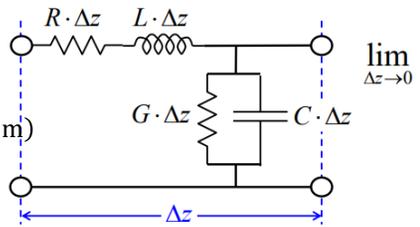


Transmission Lines

Transmission Line Model

$R \stackrel{\text{def}}{=} \text{distributed resistance } (\Omega/\text{m})$
 $L \stackrel{\text{def}}{=} \text{distributed inductance } (\text{H}/\text{m})$
 $G \stackrel{\text{def}}{=} \text{distributed conductance } (1/\Omega \cdot \text{m})$
 $C \stackrel{\text{def}}{=} \text{distributed capacitance } (\text{F}/\text{m})$



TL Equations

$$-\frac{\partial V(z,t)}{\partial z} = R \cdot I(z,t) + L \frac{\partial I(z,t)}{\partial z} \quad -\frac{\partial I(z,t)}{\partial z} = G \cdot V(z,t) + C \frac{\partial V(z,t)}{\partial z}$$

TL Wave Equations + Solutions

$$\frac{d^2 V(z)}{dz^2} - (R + j\omega L)(G + j\omega C)V(z) = 0 \quad V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

$$\frac{d^2 I(z)}{dz^2} - (R + j\omega L)(G + j\omega C)I(z) = 0 \quad I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$$

Transmission Line Parameters

Characteristic Impedance: $Z_0 = \frac{V_0^+}{I_0^+} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = R_0 + jX_0$

Complex Propagation Constant: $\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$


$$\alpha = \sqrt{\frac{RG - \omega^2 LC + \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)}}{2}}$$

$$\beta = \sqrt{\frac{-RG + \omega^2 LC + \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)}}{2}}$$

Lossless Lines ($R = G = 0$): $\alpha = 0 \quad \beta = \omega\sqrt{LC} \quad Z_0 = \sqrt{\frac{L}{C}}$

Distortionless Lines ($RC = LG$): $\alpha = \sqrt{RG} \quad \beta = \omega\sqrt{LC} \quad Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{R}{G}}$

Types of Transmission Lines

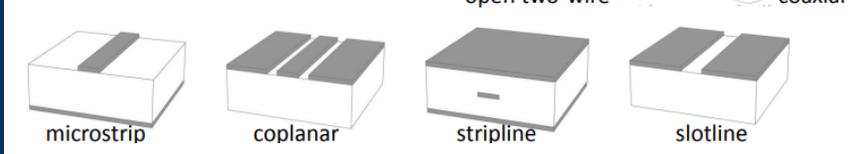

Transmission Line Behavior

General	Short	Open	Matched
Load Impedance Z_L	Load Impedance $Z_L = 0$	Load Impedance $Z_L = \infty$	Load Impedance $Z_L = Z_0$
Reflection Coefficient $\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$	Reflection Coefficient $\Gamma_L = -1$	Reflection Coefficient $\Gamma_L = +1$	Reflection Coefficient $\Gamma_L = 0$
Lossy Line $Z_{in}(\ell) = Z_0 \frac{Z_L + jZ_0 \tanh \gamma \ell}{Z_0 + jZ_L \tanh \gamma \ell}$	Lossy Line $Z_{in}(\ell) = Z_0 \tanh \gamma \ell$	Lossy Line $Z_{in}(\ell) = Z_0 \coth \gamma \ell$	Lossy Line $Z_{in}(\ell) = Z_0$
Lossless Line $Z_{in}(\ell) = Z_0 \frac{Z_L + jZ_0 \tan \beta \ell}{Z_0 + jZ_L \tan \beta \ell}$	Lossless Line $Z_{in}(\ell) = Z_0 \tan \beta \ell$	Lossless Line $Z_{in}(\ell) = -jZ_0 \cot \beta \ell$	Lossless Line $Z_{in}(\ell) = Z_0$
Standing Waves $V_{min} = V_0^+ (1 - \Gamma)$ $V_{max} = V_0^+ (1 + \Gamma)$ $I_{min} = \frac{ V_0^+ }{Z_0}(1 - \Gamma)$ $I_{max} = \frac{ V_0^+ }{Z_0}(1 + \Gamma)$ $VSWR = \frac{1 + \Gamma }{1 - \Gamma }$ $\min[Z_{in}] = Z_0/VSWR$ $\max[Z_{in}] = Z_0 \cdot VSWR$	Standing Waves $V_{min} = 0$ $V_{max} = 2 V_0^+ $ $I_{min} = 0$ $I_{max} = 2\frac{ V_0^+ }{Z_0}$ $VSWR = \infty$ $\min[Z_{in}] = 0$ $\max[Z_{in}] = \infty$	Standing Waves $V_{min} = V_0^+ $ $V_{max} = V_0^+ (1 + \Gamma)$ $I_{min} = \frac{ V_0^+ }{Z_0}(1 - \Gamma)$ $I_{max} = \frac{ V_0^+ }{Z_0}(1 + \Gamma)$ $VSWR = 1$ $\min[Z_{in}] = Z_0$ $\max[Z_{in}] = Z_0$	

Standing Waves
 $Z_{in,short} Z_{in,open} = Z_0^2 \quad P_{avg} = \frac{|V_0^+|^2}{2Z_0}(1 - |\Gamma|^2)$

Impedance Transformation

General Case (with Loss):

$$Z_{in}(\ell) = Z_0 \frac{Z_L + jZ_0 \tanh \gamma \ell}{Z_0 + jZ_L \tanh \gamma \ell}$$

Lossless Case:

$$Z_{in}(\ell) = Z_0 \frac{Z_L + jZ_0 \tan \beta \ell}{Z_0 + jZ_L \tan \beta \ell}$$

